

Experiment 1 Part 1

Aim: Verification of Maximum Power Transfer Theorem.

Theory: In a given circuit, with a load and a resultant impedance, if we want the load to have the maximum possible power transferred across it then, we need to consider the following 3 scenarios:

- 1) Only the Reactive Part of the Load can be changed.
- 2) Only the Resistive Part of the Load can be changed
- 3) Both, the Reactive and the Resistive Parts of the Load can be changed.

Case 1: Only Reactive Part (X_L) can be changed.

$$\text{Power (P)} = |I|^2 R_L$$

$$= \frac{V_s^2 \cdot R_L}{(R_i^2 + R_L)^2 + (X_i + X_L)^2}$$

$$(R_i^2 + R_L)^2 + (X_i + X_L)^2$$

For P to be max, $(X_i + X_L)^2$ should be minimum. Thus,

$$(X_i + X_L)^2 = 0$$

$$\Rightarrow X_L = -X_i \quad \text{--- (1)}$$

Case 2: Only Resistive Part (R_L) can be changed.

$$P = \frac{V_s^2 R_L}{(R_i^2 + R_L)^2 + (X_i + X_L)^2}$$

$$(R_i^2 + R_L)^2 + (X_i + X_L)^2$$

Differentiating P w.r.t. R_L and equating $\frac{dP}{dR_L} = 0$

$$\Rightarrow \text{we get } R_L = \sqrt{R_i^2 + (X_i + X_L)^2} \quad \text{--- (2)}$$

Case 3: Both X_L and R_L can be changed


Then we put $X_L = -X_i$ --- from (1)


and from (2), $R_L = R_i$

This can also be achieved by putting $Z_L = Z_i^*$
where Z_i^* is the complex conjugate of Z_i .

Kaushal
Bansal

19CS10039

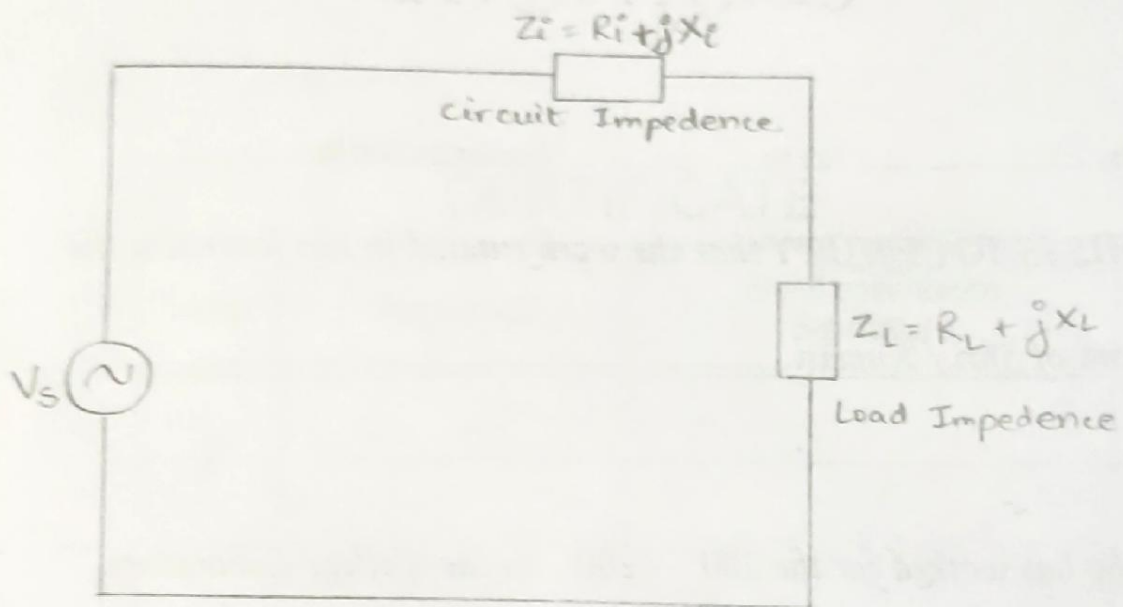

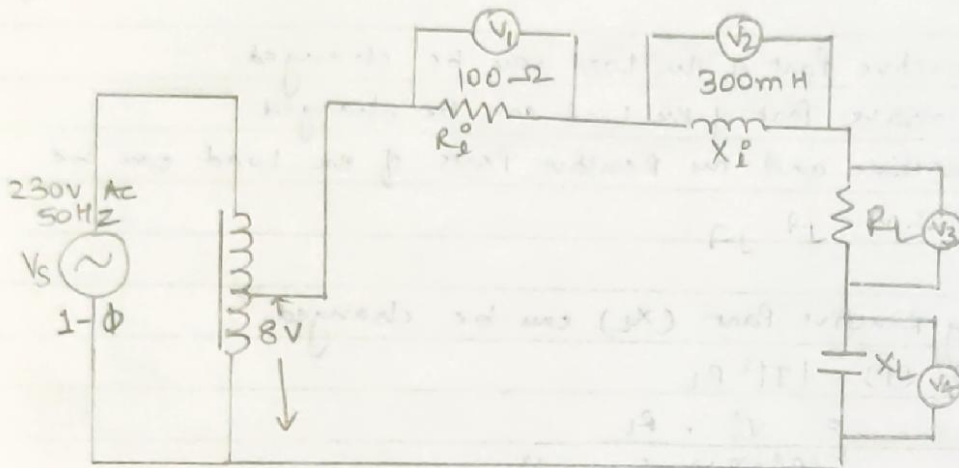

Observation Tables : (for $k = 0.99$)

Case 1 : Only C_L / C_L variable, with $R_L = 50 \Omega$

Sl. No.	C_L (in μF)	V_1 (in V)	V_3 (in V)	$(V_1 \cdot V_3)$ (in V^2)	Maximum ($V_1 \cdot V_3$)
1.	25	5.242	2.620	13.734	
2.	28	5.298	2.657	14.077	
3.	30	5.309	2.654	14.090	
4.	33.77	5.315	2.652	14.095	$\Rightarrow 14.095 V^2$ for $C_L = 33.77 \mu F$
5	35	5.300	2.649	14.041	
6	38	5.269	2.635	13.886	
7	40	5.238	2.620	13.717	
8	45	5.190	2.593	13.460	

\therefore value of C_L for maximum power transfer = 33.77 μF .

Case 2 : Only R_L variable, with $C_L = 50 \mu F$

Sl. No.	R_L (in Ω)	V_1 (in V)	V_3 (in V)	$(V_1 \cdot V_3)$ (in V^2)	Maximum ($V_1 \cdot V_3$)
1	95	3.999	3.800	15.198	
2	98	3.939	3.860	15.205	
3	100	3.901	3.901	15.221	
4	104.57	3.817	3.990	15.230	$\Rightarrow 15.230 V^2$ for $R_L = 104.57 \Omega$
5	108	3.746	4.049	15.168	
6	110	3.711	4.080	15.141	
7	115	3.635	4.179	15.191	
8	120	3.556	4.268	15.177	

\therefore value of R_L for maximum power transfer = 104.57 Ω

Case 3: Both R_L and X_L/C_L variable:

Sl. No.	R_L (in Ω)	C_L (in μF)	V_1 (in V)	V_3 (in V)	(V_1, V_3) (in V^2)	Maximum (V_1, V_3)
1	80	25	4.385	3.508	15.383	
2	90	28	4.187	3.776	15.810	
3	95	30	4.083	3.878	15.834	
4	100	33.77	3.988	3.988	15.904	$\Rightarrow 15.904 V^2$ for $R_L = 100 \Omega$
5	105	35	3.871	4.074	15.770	and $C_L = 33.77 \mu F$.
6	110	40	3.765	4.150	15.624	
7	120	45	3.579	4.297	15.379	
8	125	48	3.490	4.361	15.230	

\therefore Value of $R_L = 100 \Omega$ and $C_L = 33.77 \mu F$, for maximum power transfer.

Inference and Sample Calculations:

For Case 1, $C_L = 33.77 \mu F$, which is the same value that comes when we equate $|X_C| = |X_L|$

$$\Rightarrow C = \frac{1}{\omega^2 L} = \frac{1}{4\pi^2 f^2 L} = \frac{1}{4\pi^2 (50)^2 (300) \times 10^{-3}}$$

$$= 33.77 \times 10^{-6} F.$$

Also, here $V_2 = 4.97 V$

and $V_4 = 4.97 V \therefore V_2 = V_4$

For Case 2, $R_L = 104.57 \Omega$, which is the same value that comes when we equate $R = \sqrt{R_i^2 + (X_i + X_L)^2}$

$$= \sqrt{(100)^2 + (800 \times 10^{-3} \times 2\pi \times 50 - \frac{1}{50 \times 10^{-6} \times 2\pi \times 50})^2}$$

$$= \sqrt{10000 + (94.248 - 63.662)^2}$$

$$= \sqrt{10000 + 935.505}$$

$$= 104.57 \Omega$$

For case 3, $R_L = 100 \Omega$ and $C_L = 33.77 \mu F$, which are the same values we get when ~~do~~ equate

$$R = R_i = 100 \Omega \quad \text{and} \quad |X_i| = |X_L|$$

$$\Rightarrow C = \frac{1}{L\omega^2} = 33.77 \mu F$$

$$\text{Also, } V_1 = 3.988 V$$


$$\text{and } V_3 = 3.988 V \quad \therefore V_1 = V_3$$

$$\text{Also, } V_2 = 3.701$$

$$V_4 = 3.701 V \quad \therefore V_2 = V_4$$

Discussion and Comments: from the above experiment, we have understood that for maximum power to be transferred through a load ~~resistance~~ impedance, we need to consider 3 cases and appropriately set up the values of load parameters.

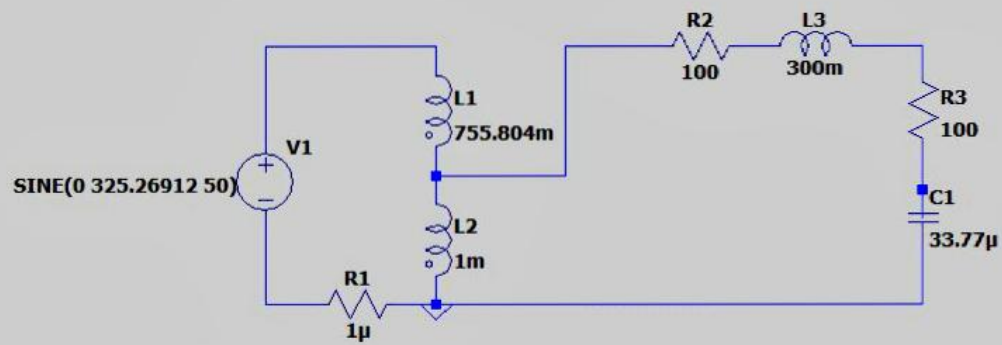One point to note, while doing this experiment in the LTSpice Environment, is that the environment gives waveforms and we have to take amplitude of the waveforms and then calculate the RMS values from it. It doesn't directly give the RMS values.



K L1 L2 0.99
.tran 0 20 0 1