

Experiment 1 Part 2

Aim: Verification of Reciprocity Theorem.

Theory: The reciprocity theorem states that if an emf E in one branch ~~to~~ of a reciprocal network produces a current I in another, then if the emf E is moved from the first branch to the second branch, it will cause the same current in the first branch, where the emf now has been replaced by a short circuit.

A general formula can be written as

$$\frac{V_1}{I_2} = \frac{V_2}{I_1}, \text{ where } V_1 \text{ is emf in first branch and}$$

other branch is short circuited,
 I_1 is current in the second branch,
when V_1 is the emf in the first branch

V_2 is emf in second branch and
first branch is short circuited,
 I_2 is current in the first branch,
when V_2 is the emf in the second branch.

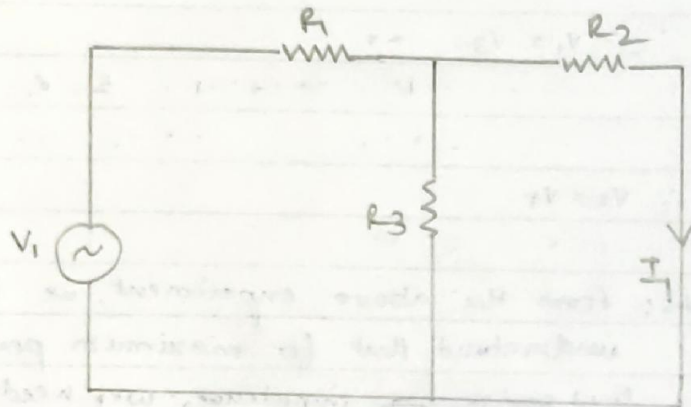


Fig. 1



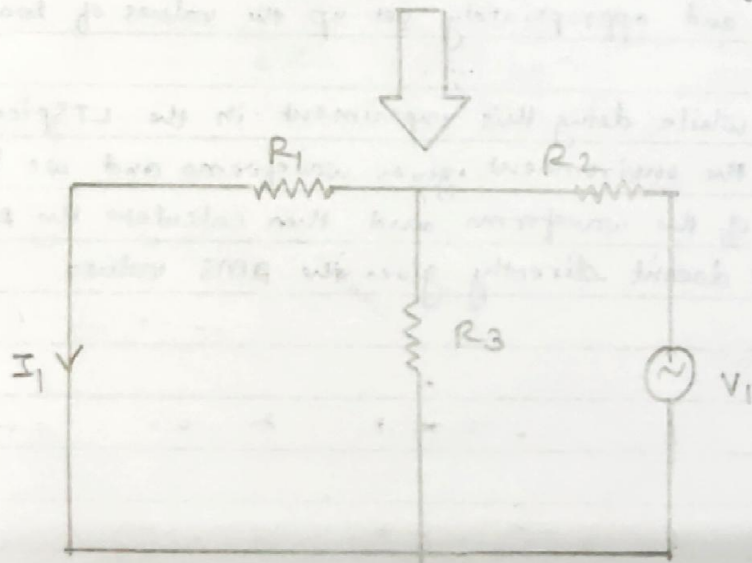


Fig. 2

Figure 1 implies Figure 2.

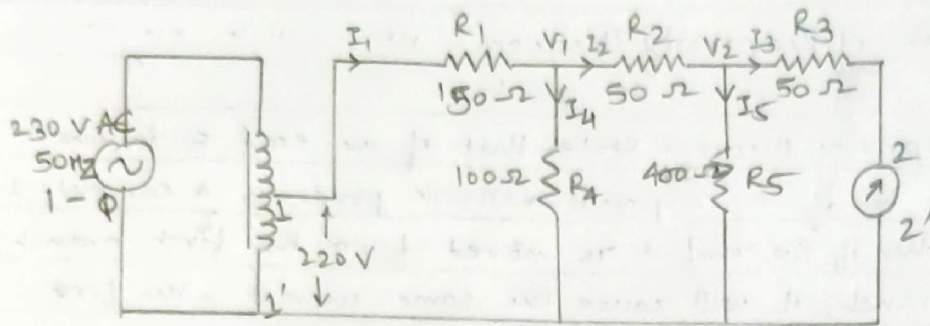

Circuit 1

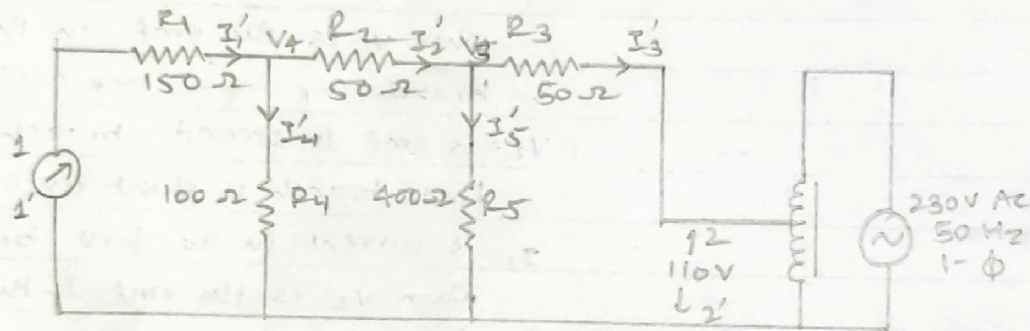

Circuit 2.

Observation Table: (for $k = 0.99$)

V_s (V)	I_3 (A)	V_s / I_3 (V/A)	V_s' (V)	I_1' (A)	V_s' / I_1' (V/A)
220	0.504	436.51	110	0.252	436.51

Also, $I_1 = 1.088 \text{ A}$

$I_1' = \cancel{0.252 \text{ A}} 0.252 \text{ A}$

$I_2 = 0.561 \text{ A}$

$I_2' = 0.631 \text{ A}$

$I_3 = 0.504 \text{ A}$

$I_3' = 0.804 \text{ A}$

$I_4 = 0.527 \text{ A}$

$I_4' = 0.378 \text{ A}$

$I_5 = 0.063 \text{ A}$

$I_5' = 0.173 \text{ A}$

$V_1 = 53.45 \text{ V}$

$V_3 = 69.23 \text{ V}$

$V_2 = 25.17 \text{ V}$

$V_4 = 37.82 \text{ V}$

Inference and Sample Calculation:


Here we can see that, $\frac{V_s}{I_3} = \frac{V_s'}{I_1'} = 436.51 \frac{\text{V}}{\text{A}}$

Discussion and Comments: After performing the above experiment, we can conclude that reciprocity theorem


is valid and that it can be generalised into the formula of

$\frac{V_s}{I_3} = \frac{V_s'}{I_1'}$ for different voltages too.

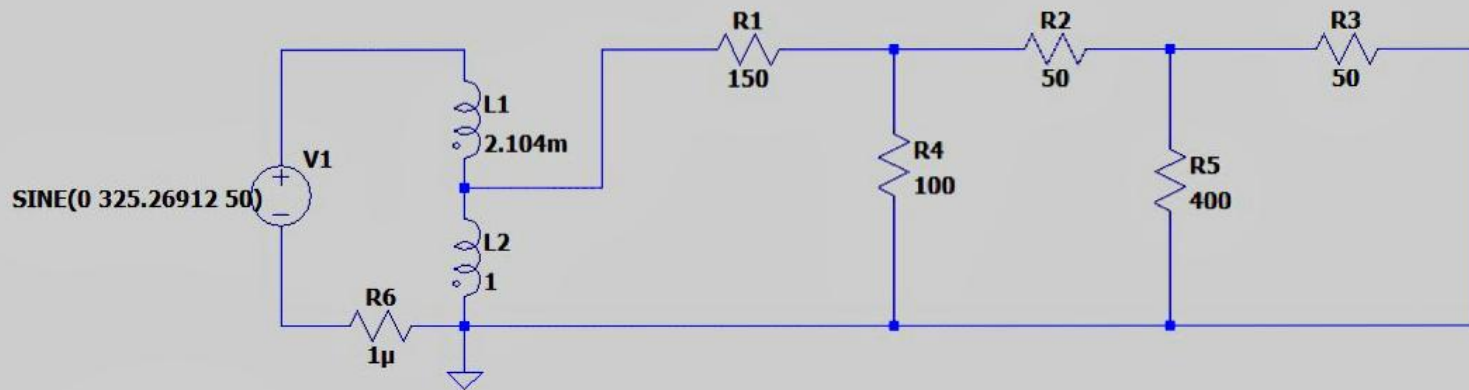One point to note is that, there is no component of ammeter, so to measure the current, in circuit 1, the current is measured across R_3 (for I_3) and in circuit 2, the current is measured across R_1 (for I_1').



K L1 L2 0.99
.tran 0 5 0 1

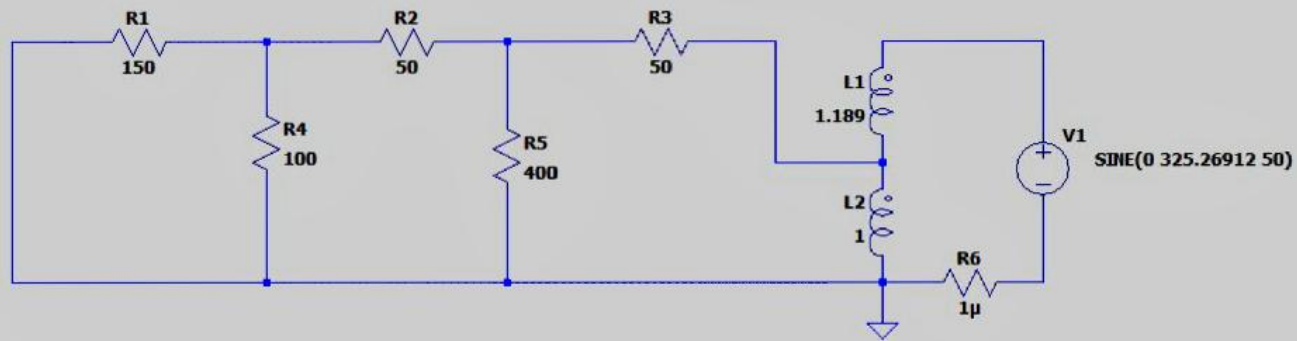

```

K L1 L2 0.99
.tran 0 5 0 1
    
```