

Experiment 2 Part 2

Q2

Aim: To solve an RLC circuit (with initial conditions) and find the voltage across the capacitor and the current across the inductor as a function of time.

(A) Here the initial conditions are again relaxed, with $v(0^-) = 0$ and $i(0^-) = 0$. Also, since $L \frac{di(t)}{dt} = v(t) \therefore v(0^-) = \frac{di}{dt}(0^-) = 0$

Using Kirchhoff's Voltage Law, we get

$$20 - R(i_R(t)) - L \frac{di(t)}{dt} = 0 \quad \text{--- (1)}$$

and

$$\frac{L di(t)}{dt} - v(t) = 0 \Rightarrow \frac{L di(t)}{dt} = v(t) \Rightarrow L \frac{d^2 i(t)}{dt^2} = \frac{dv(t)}{dt} \quad \text{--- (2)}$$

From Kirchhoff's Current Law, we get,

$$i_R(t) = i(t) + i_C(t) \quad \text{--- (3)}$$

Also, we have

$$i_C(t) = C \frac{dv(t)}{dt} \quad \text{--- (4)}$$

From (1) and (3)

$$\Rightarrow 20 - R \left[i(t) + i_C(t) \right] - L \frac{di(t)}{dt} = 0 \quad \text{--- (5)}$$

From (4) and (5)



$$20 - R \left[i(t) + C \frac{dv(t)}{dt} \right] - L \frac{di(t)}{dt} = 0 \quad \text{--- (6)}$$

From (2) and (6)

$$20 - R \left[i(t) + C \cdot L \frac{d^2 i(t)}{dt^2} \right] - L \frac{di(t)}{dt} = 0$$

$$\Rightarrow 20 - 2 \left[i(t) + C \cdot (2) \frac{d^2 i(t)}{dt^2} \right] - 2 \frac{di(t)}{dt} = 0$$
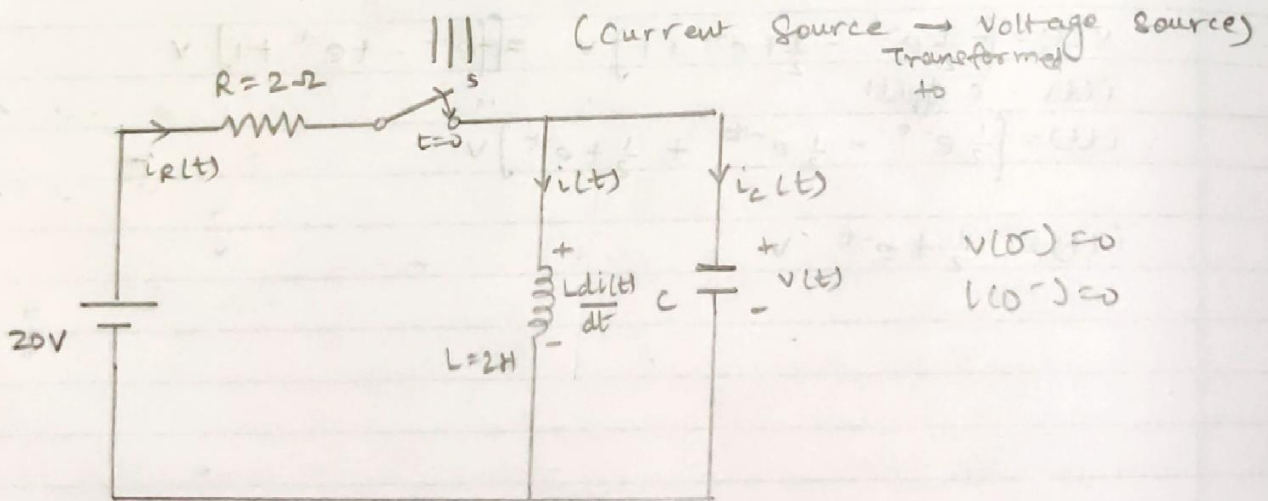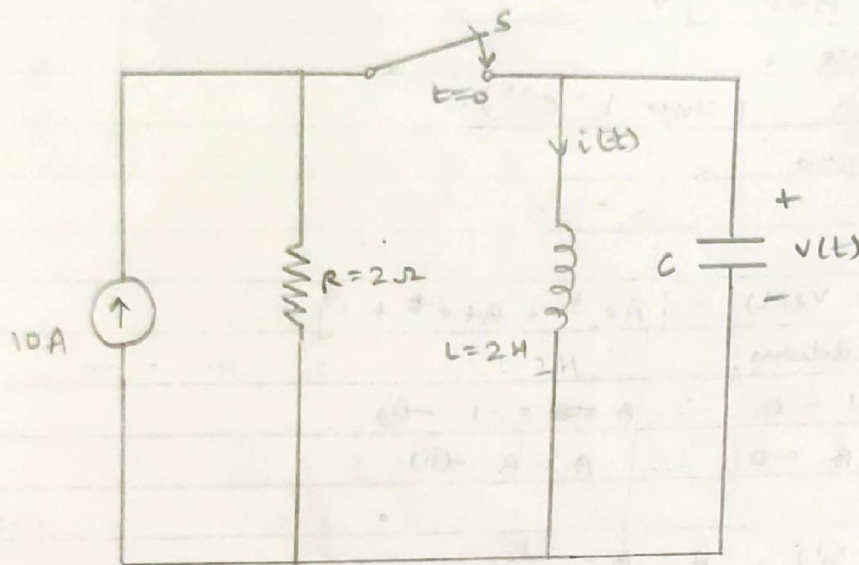
$$\Rightarrow 4C \frac{d^2 i(t)}{dt^2} + 2 \frac{di(t)}{dt} + 2i(t) = 20 \Rightarrow \frac{d^2 i(t)}{dt^2} + \frac{1}{2C} \frac{di(t)}{dt} + \frac{1}{2C} i(t) = \frac{5}{C} \quad \text{--- (7)}$$



→ For (i), $C = \frac{1}{9} F$

∴ From (d'), we get

$$\boxed{\frac{d^2 i(t)}{dt^2} + 9 \cdot \frac{di(t)}{2 dt} + \frac{9}{2} i(t) = 45} \Rightarrow \left(D^2 + \frac{9}{2} D + \frac{9}{2}\right) i(t) = 45$$

Characteristic equation $\Rightarrow m^2 + \frac{9}{2} m + \frac{9}{2} = 0$

$$\Rightarrow (m+3) \left(m + \frac{3}{2}\right) = 0$$

$$\therefore m = -3, -\frac{3}{2}$$

The roots are real and distinct

∴ The complementary solution (natural response) is

$$i_n(t) = [A e^{-3t} + B e^{-\frac{3}{2}t}] A$$

The forced response is

$$i_f(t) = \frac{45}{9/2} \quad (\text{since } 45 = 45 e^{0t})$$

$$\left(D^2 + \frac{9}{2} D + \frac{9}{2}\right) \Big|_{D=0}$$

$$i_f(t) = \frac{45}{9/2} A = 10 A$$

$$\therefore i(t) = i_n(t) + i_f(t) = [A e^{-3t} + B e^{-\frac{3}{2}t} + 10] A$$

Using initial conditions,

$$i(0) = A + B + 10 = 0 \quad \text{--- (i)}$$

$$\frac{di(0)}{dt} = -3A - \frac{3}{2} B = 0 \quad \Rightarrow 2A + B = 0 \quad \text{--- (ii)}$$

$$\text{from (i) and (ii), } A = 10 \quad \therefore B = -20$$

$$\begin{aligned} \therefore i(t) &= [10 e^{-3t} - 20 e^{-\frac{3}{2}t} + 10] A = 10 [e^{-3t} - 2e^{-\frac{3}{2}t} + 1] A \\ &= 10 [e^{-\frac{3}{2}t} - 1]^2 A \end{aligned}$$

$$v(t) = L \frac{di(t)}{dt} = 2 \left[10 \cdot 2 (e^{-\frac{3}{2}t} - 1) \cdot \left(-\frac{3}{2}\right) e^{-\frac{3}{2}t} \right] v.$$

$$v(t) = -60 (e^{-3t} - e^{-\frac{3}{2}t}) v$$

→ For (ii), $C = \frac{1}{4} F$

From (9), we get,

$$\frac{d^2 i(t)}{dt^2} + 2 \frac{di(t)}{dt} + 2 i(t) = 20 \Rightarrow (D^2 + 2D + 2) i(t) = 20$$

$$\text{Characteristic equation} \Rightarrow m^2 + 2m + 2 = 0$$

$$\Rightarrow (m+1)^2 = -1$$

$$\therefore m = -1 \pm j$$

The roots are complex and distinct.

The complementary solution (natural response)

$$i_n(t) = [A e^{(-1+j)t} + B e^{(-1-j)t}] A$$

The forced response is

$$i_f(t) = \frac{20}{(D^2 + 2D + 2)} \Big|_{D=0} \quad (\text{Since } 20 = 20e^{0t})$$

$$i_f(t) = 10 A$$

$$\therefore i(t) = i_n(t) + i_f(t) = [A e^{(-1+j)t} + B e^{(-1-j)t} + 10] A$$

Using Initial conditions,

$$i(0) = A + B + 10 = 0 \Rightarrow A = -10 - B \quad (i)$$

$$\frac{di(0)}{dt} = (-1+j)A + (-1-j)B = 0 \quad (ii)$$

From (i) and (ii),

$$(-1+j)(-10-B) - (1+j)B = 0$$

$$\Rightarrow 10(1-j) + B(1-j) - (1+j)B = 0$$

$$\Rightarrow 10(1-j) = 2jB$$

$$\therefore B = \frac{10(1-j)}{2j} = 5 \left(\frac{1-j}{j} \right) = 5(-j-1)$$

$$\therefore A = -10 - B = -10 - 5(-j-1) = -10 + 5(j+1) = -5 + 5j$$

$$\therefore A = 5(j-1)$$

$$\begin{aligned} \therefore i(t) &= [5(j-1)e^{(-1+j)t} + 5(-j-1)e^{(-1-j)t} + 10] A \\ &= 5 \left[e^{-t} (j e^{jt} - e^{-jt} - j e^{-jt} - e^{jt}) + 2 \right] A \\ &= 5 \left[e^{-t} (-e^{jt} - e^{-jt} + j e^{jt} - j e^{-jt}) + 2 \right] A \\ &= 10 \left[-e^{-t} \left(\frac{e^{jt} + e^{-jt}}{2} \right) + \left(\frac{e^{jt} - e^{-jt}}{2j} \right) \right] + 2 \right] A \end{aligned}$$

$$\therefore i(t) = 10 \left[-e^{-t} (\cos t + 8 \sin t) + 1 \right] = -10e^{-t} [\sin t + \cos t - e^t]$$

$$\therefore v(t) = L \frac{di(t)}{dt} = 2 \left[10 \cdot (-e^{-t} \cos t + e^{-t} \sin t) \right]$$

$$\therefore v(t) = -20 [\sin t + \cos t]$$

$$\begin{aligned} \therefore v(t) &= L \frac{di(t)}{dt} = 2(-10) \left[-e^{-t} (\sin t + \cos t - e^t) + e^{-t} (\cos t - \sin t - e^t) \right] \\ &= -20 \left[-2e^{-t} \sin t \right] \\ &= 40e^{-t} \sin t \end{aligned}$$

→ For (iii), $C = \frac{1}{8} F$

from (or), we get

$$\left[\frac{d^2 i(t)}{dt^2} + 4 \frac{di(t)}{dt} + 4 i(t) = 40 \right] \Rightarrow (D^2 + 4D + 4) i(t) = 40$$

Characteristic Equation $\Rightarrow m^2 + 4m + 4 = 0$

$$\Rightarrow (m+2)^2 = 0$$

$$\therefore m = -2, -2$$

The roots are real and equal.

\therefore The complementary solution (natural response)

$$i_n(t) = [Ae^{-2t} + Bte^{-2t}] A$$

The forced response is

$$i_f(t) = \frac{40}{(D^2 + 4D + 4)} \Big|_{D=0} \quad (\text{Since } 40 = 40e^{0t})$$

$$\therefore i_f(t) = \frac{40}{4} = 10 A$$

$$\therefore i(t) = i_n(t) + i_f(t) = [Ae^{-2t} + Bte^{-2t} + 10] A$$

Using initial conditions

$$i(0^-) = A + 10 = 0 \quad \therefore A = -10$$

$$\frac{di(0^-)}{dt} = -2A + B = 0 \quad \therefore 2A = B \quad \therefore B = -20$$


$$\therefore i(t) = [-10e^{-2t} - 20te^{-2t} + 10] A = -10[e^{-2t} + 2te^{-2t} - 1] A$$



$$\therefore v(t) = L \frac{di(t)}{dt} = 2[-10(-2e^{-2t} + 2e^{-2t} - 4te^{-2t})] = 80te^{-2t} V$$



$V(t)$ and $i(t)$ vs t for Q2(A)


Kaushal Banthia 19CS10039

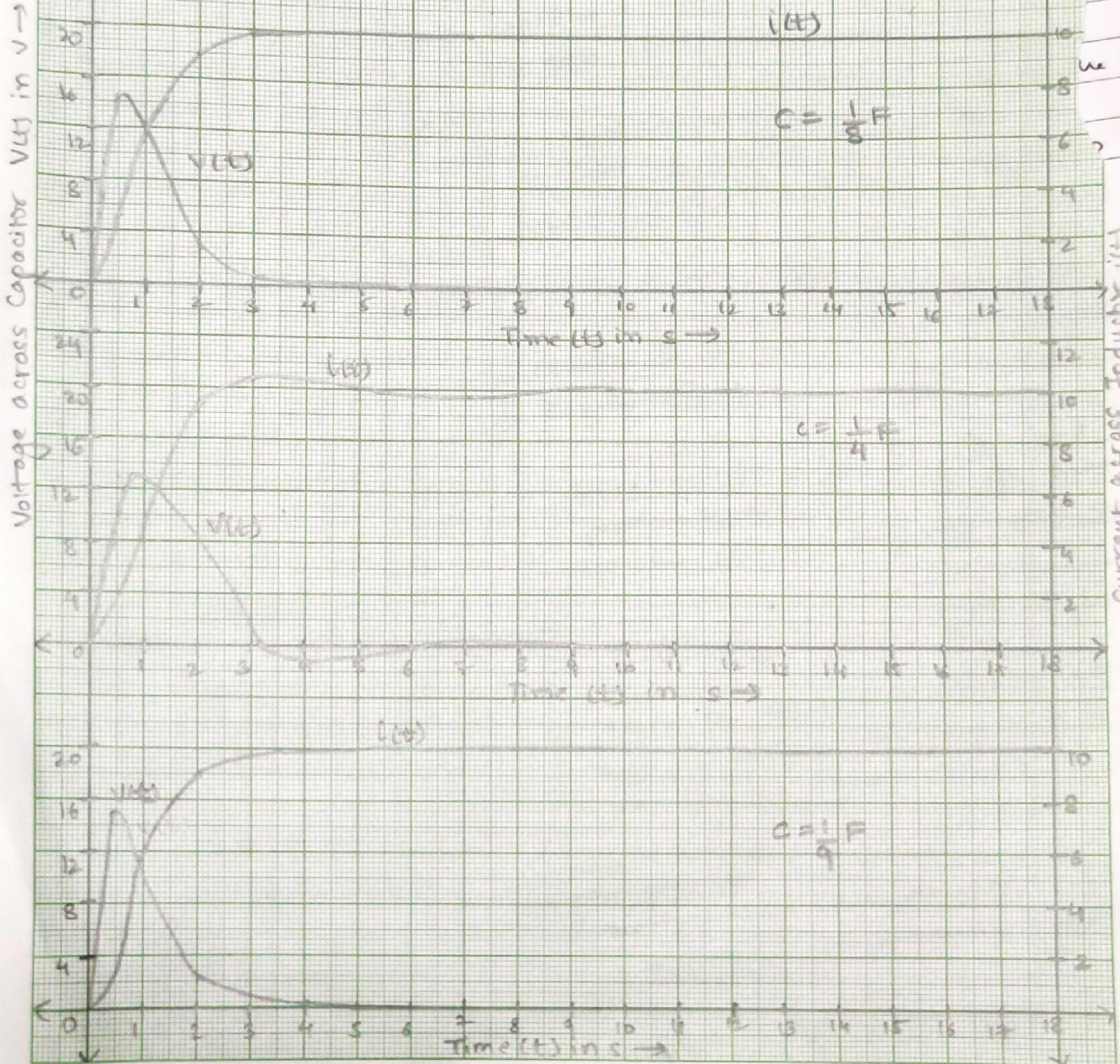Scale:
On x-axis:
1cm = 1s
On y-axis:
Left: 1cm = 4V
Right: 1cm = 2A



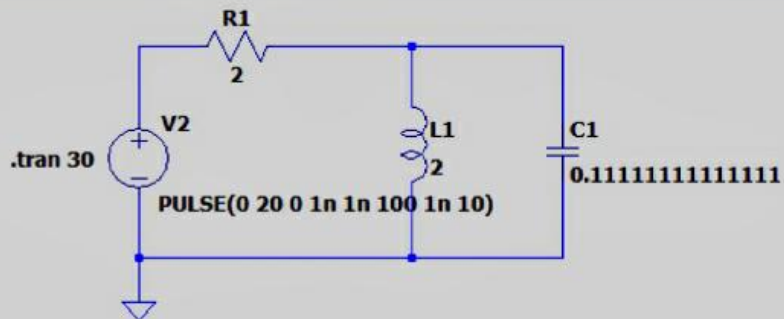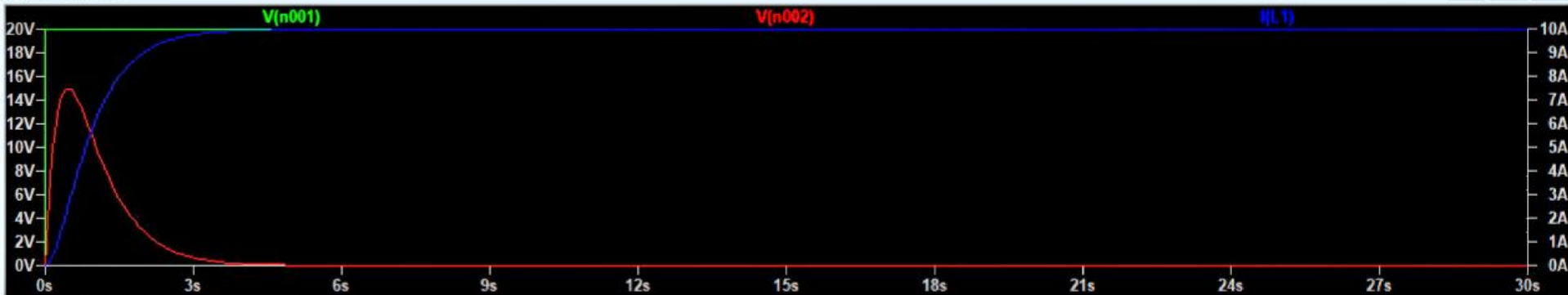

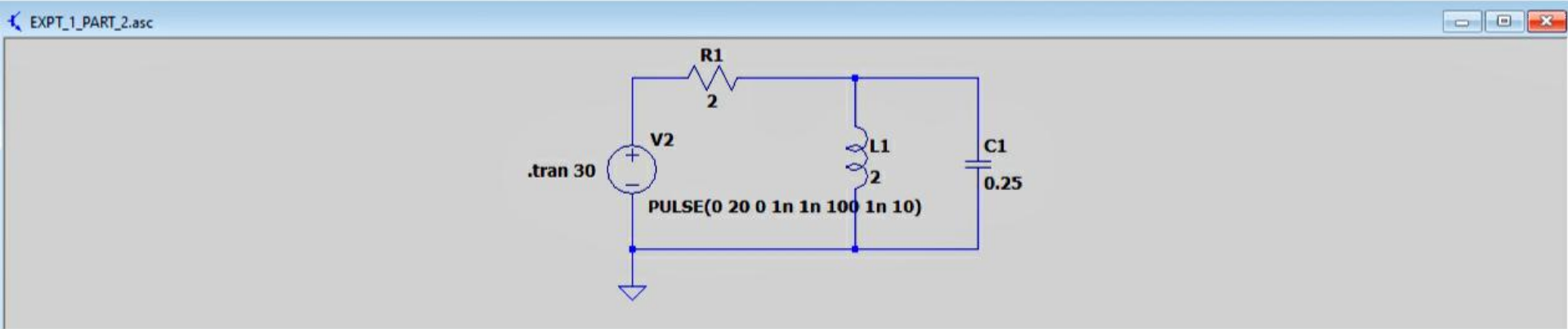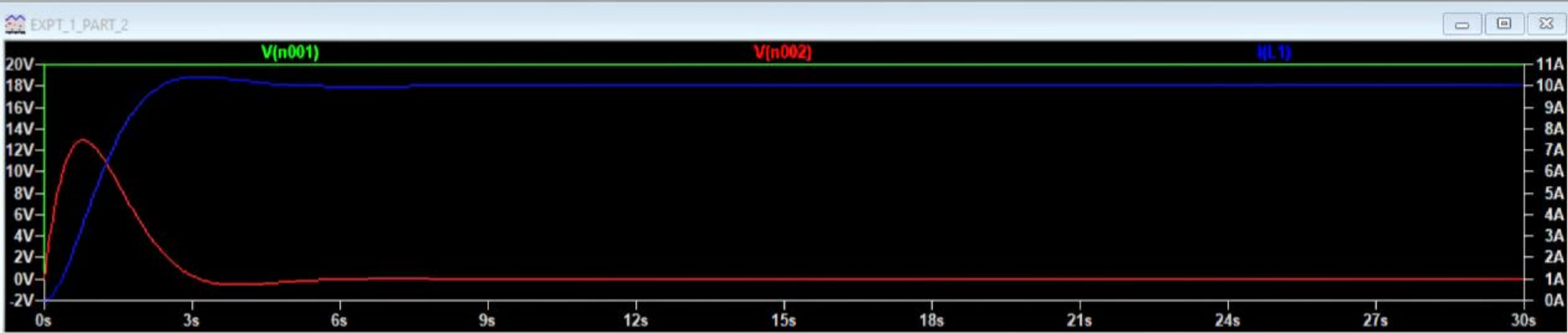

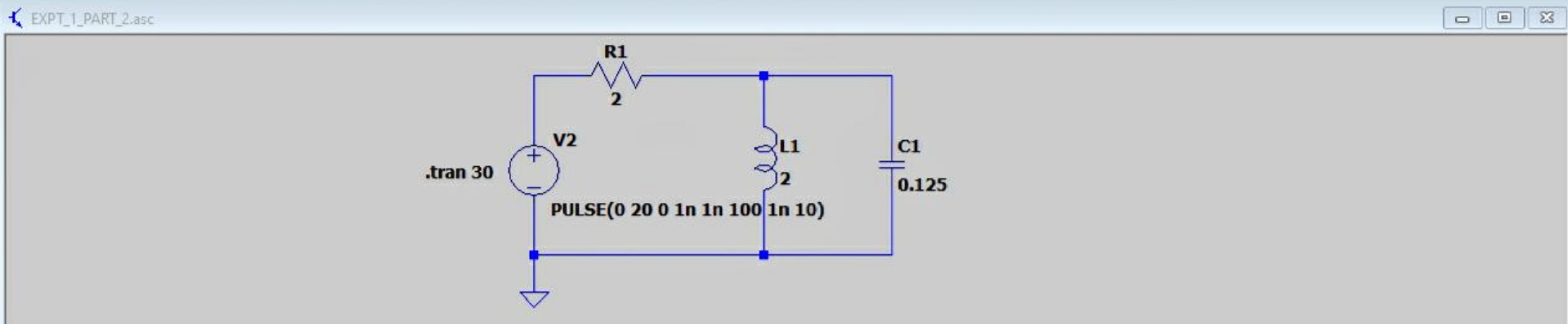

(B) Here since $V(0^-) = 5V$, thus we attach a $5V$ ^{DC} source to the capacitor in series and consider it unchanged, i.e., $V_c(0^-) = 0$.
Here ~~$i(0^-)$~~ $i(0^-) = 0$.

The equations would be similar ~~to~~ to the previous with the exception of equation number (2)

\Rightarrow Equation (1) $\Rightarrow 20 - R i(t) - L \frac{di(t)}{dt} = 0$ — (1)'

Also, we have $\Rightarrow L \frac{di(t)}{dt} = 5 + V_c(t) \Rightarrow L \frac{d^2 i(t)}{dt^2} = \frac{dV_c(t)}{dt}$
(This gives $\frac{di}{dt}(0^-) = \frac{5}{L}$) — (2)'

From Equation (3) $\Rightarrow i(t) = i_L(t) + i_c(t)$ — (3)


From Equation (4) $\Rightarrow i_c(t) = C \frac{dV_c(t)}{dt}$ — (4)'

Since equations (1)', (2)', (3)' and (4)' are same as the previous equations (1), (2), (3), (4) from part (A), we know that the corresponding differential equations will also be the same.

\therefore we get $\frac{d^2 i(t)}{dt^2} + \frac{1}{2C} \frac{di(t)}{dt} + \frac{1}{2C} i(t) = \frac{5}{C}$ — (B)

Since the differential equation is the same, we can also say that the solutions are going to be the same too, for parts (i), (ii), (iii), i.e., for the various values of the capacitors.


Kaushal Banthia
19CS10039

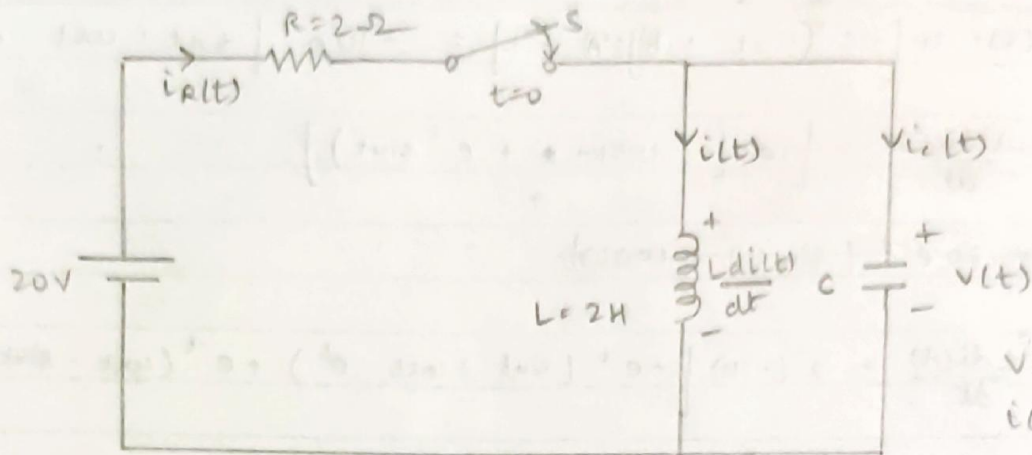

$$v_L(0^-) = 5V$$

$$i_C(0^-) = 0$$

|||

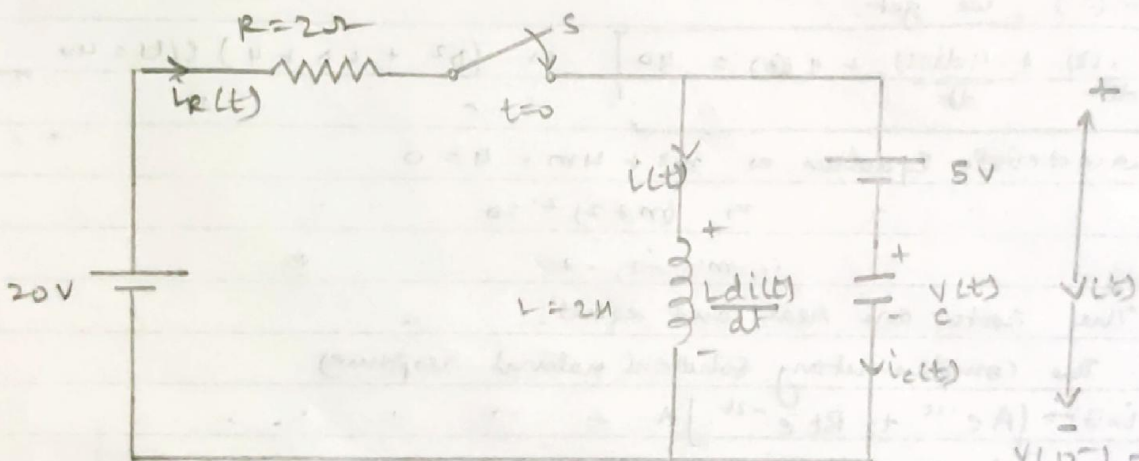

$$v_L(0^+) = 0V$$

$$i_C(0^+) = 0$$

→ For part (i), $c = \frac{1}{9} F$

From (B), we get

$$\frac{d^2 i(t)}{dt^2} + \frac{9}{2} \frac{di(t)}{dt} + \frac{9}{2} i(t) = 45 \Rightarrow (D^2 + \frac{9}{2} D + \frac{9}{2}) i(t) = 45$$

The characteristic equation is the same as before in part A (i)

$$\therefore m = -3, -\frac{3}{2}$$

$$\therefore \text{Natural response in } i(t) = [Ae^{-3t} + Be^{-\frac{3t}{2}}] A$$

$$\text{Forced Response} = \frac{45}{D^2 + \frac{9}{2} D + \frac{9}{2}} \quad (\text{Since } 45 = 45e^{0t})$$

$$i_f(t) (D^2 + \frac{9}{2} D + \frac{9}{2}) \Big|_{D=0}$$

$$i_f(t) = 10 A$$

$$\therefore i(t) = i_n(t) + i_f(t) = [Ae^{-3t} + Be^{-\frac{3t}{2}} + 10] A$$

$$\text{Now } i(0^-) = A + B + 10 = 0 \Rightarrow 6A + 6B = -60 \quad \text{--- (i)}$$

$$\frac{di(0^-)}{dt} = \frac{-3A - \frac{3B}{2}}{2} = \frac{5}{2} \Rightarrow 6A + 3B = -5 \quad \text{--- (ii)}$$

$$\therefore 3B = -55 \Rightarrow B = \frac{-55}{3} \Rightarrow A = \frac{25}{3}$$

$$\therefore i(t) = \left[\frac{25}{3} e^{-3t} - \frac{55}{3} e^{-\frac{3t}{2}} + 10 \right] A$$

$$\text{Now } \frac{L di(t)}{dt} = 2 \left[-25e^{-3t} + \frac{55}{2} e^{-\frac{3t}{2}} \right] = 5 + v_o(t) = v(t)$$

$$\therefore \cancel{v(t)} = \left[\cancel{-50e^{-3t}} + \frac{55}{2} e^{-\frac{3t}{2}} \right] V$$

$$v(t) = \left[-50e^{-3t} + 55 e^{-\frac{3t}{2}} \right] V$$

→ For part (ii), $c = \frac{1}{4} F$

$$\text{From (B), we get } \frac{d^2 i(t)}{dt^2} + 2 \frac{di(t)}{dt} + 2 i(t) = 20 \Rightarrow (D^2 + 2D + 2) i(t) = 20$$

characteristic equation is the same as before in part A (ii)

$$\therefore m = -1 \pm j$$

$$\therefore \text{Natural Response } i_n(t) = [Ae^{(-1+j)t} + Be^{(-1-j)t}] A$$

$$\text{Forced Response} = \frac{20}{D^2 + 2D + 2} \quad (\text{Since } 20 = 20e^{0t})$$

$$i_f(t) (D^2 + 2D + 2) \Big|_{D=0}$$

$$i_f(t) = 10 A$$

$$i(t) = i_n(t) + i_f(t) = [A e^{(-1+j)t} + B e^{(-1-j)t} + 10] A$$

$$\text{Now } i(0^-) = A + B + 10 = 0 \Rightarrow A = -B - 10 \quad \text{---(i)}$$

$$\frac{di(0^-)}{dt} = (-1+j)A - (1+j)B = \frac{5}{2} \quad \text{---(ii)}$$

From (i) and (ii),

$$(-1+j)(-B-10) - (1+j)B = \frac{5}{2}$$

$$\Rightarrow B(1-j) + 10(1-j) - (1+j)B = \frac{5}{2}$$

$$\Rightarrow -2jB + 10 - 10j = \frac{5}{2}$$

$$\Rightarrow -4jB + 20 - 20j = \frac{5}{2}$$

$$\Rightarrow 4jB = 15 - 20j$$

$$\Rightarrow B = \frac{15 - 20j}{4j} = \frac{(-15j - 20)}{4}$$

$$\therefore A = -B - 10 = \frac{-15j + 20 - 40}{4} = \frac{15j - 20}{4}$$

$$\therefore i(t) = \left[\frac{(15j - 20)}{4} e^{(-1+j)t} - \left(\frac{15j + 20}{4} \right) e^{(-1-j)t} + 10 \right] A$$

$$= e^{-t} \left[\frac{15j}{4} e^{jt} - 5e^{jt} - \frac{15j}{4} e^{-jt} - 5e^{-jt} + 10e^t \right] A$$

$$= e^{-t} \left[-\frac{15}{2} \left(\frac{e^{jt} - e^{-jt}}{2j} \right) - 5 \left(\frac{e^{jt} + e^{-jt}}{2} \right) \times 2 + 10e^t \right] A$$

$$= e^{-t} \left[-\frac{15}{2} \sin t - 10 \cos t + 10e^t \right] A$$

$$i(t) = \frac{-5}{2} e^{-t} [3 \sin t + 4 \cos t - 4e^t] A$$

$$\begin{aligned} \text{Now, } \mathcal{L} \left(\frac{di(t)}{dt} \right) &= (2) \frac{5}{2} \int_0^- e^{-t} [3 \sin t + 4 \cos t - 4e^t] - \frac{5}{2} e^{-t} [3 \cos t - 4 \sin t - 4e^t] A \\ &= 5 e^{-t} [7 \sin t + \cos t] = v_e(t) + 5 = v(t) \end{aligned}$$

$$\therefore v(t) = 5 e^{-t} [7 \sin t + \cos t] v$$

→ For (iii), $c = \frac{1}{8} F$

from β , we get

$$\frac{d^2 i(t)}{dt^2} + 4 \frac{di(t)}{dt} + 4 i(t) = 40 \quad \Rightarrow (D^2 + 4D + 4) i(t) = 40$$

The characteristic equation is the same as before in part A (iii)

$$\therefore m = -2, -2$$

$$\therefore \text{Natural Response } i_n(t) = [A e^{-2t} + B t e^{-2t}] A$$

$$\text{Forced Response } i_f(t) = \frac{40}{(D^2 + 4D + 4)} \Big|_{D=0} \quad (\text{since } 4D = 40 e^{0t})$$

$$i_f(t) = 10 A$$

$$\therefore i(t) = i_n(t) + i_f(t) = [A e^{-2t} + B t e^{-2t} + 10] A$$

Now,

$$i(0^-) = A + 10 = 0 \quad \Rightarrow A = -10$$

$$\frac{di(0^-)}{dt} = -2A + B = \frac{5}{2} \quad \Rightarrow -2(-10) + B = \frac{5}{2}$$

$$\Rightarrow 20 + B = \frac{5}{2}$$

$$\Rightarrow B = -\frac{35}{2}$$

$$\therefore i(t) = [-10 e^{-2t} - \frac{35}{2} t e^{-2t} + 10] A$$

$$\therefore \text{Now, } L \frac{di(t)}{dt} = 2 \left[20 e^{-2t} - \frac{35}{2} e^{-2t} + 35 t e^{-2t} \right] \times$$

$$= 2 \left[\frac{5}{2} e^{-2t} + 35 t e^{-2t} \right]$$

$$= \left[e^{-2t} \right] [5 + 70t] = v_c(t) + 5$$

$$= v(t)$$

$$\therefore v(t) = e^{-2t} (5 + 70t) V$$




$$v(t) = e^{-2t} (5 + 70t) V.$$

$V(t)$ and $i(t)$ v time for Q2(B)



Kaushal Bantua
19CS10039



Scale:
On x axis:
 $1\text{cm} = 1\text{s}$
On y axis:
Left: $1\text{cm} = 4\text{V}$
Right: $1\text{cm} = 2\text{A}$

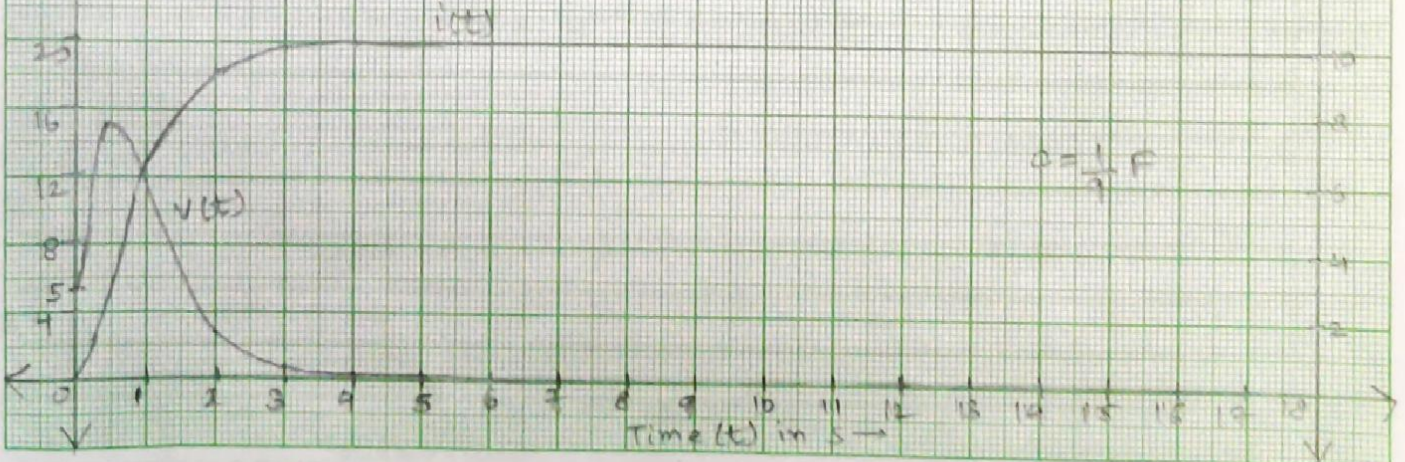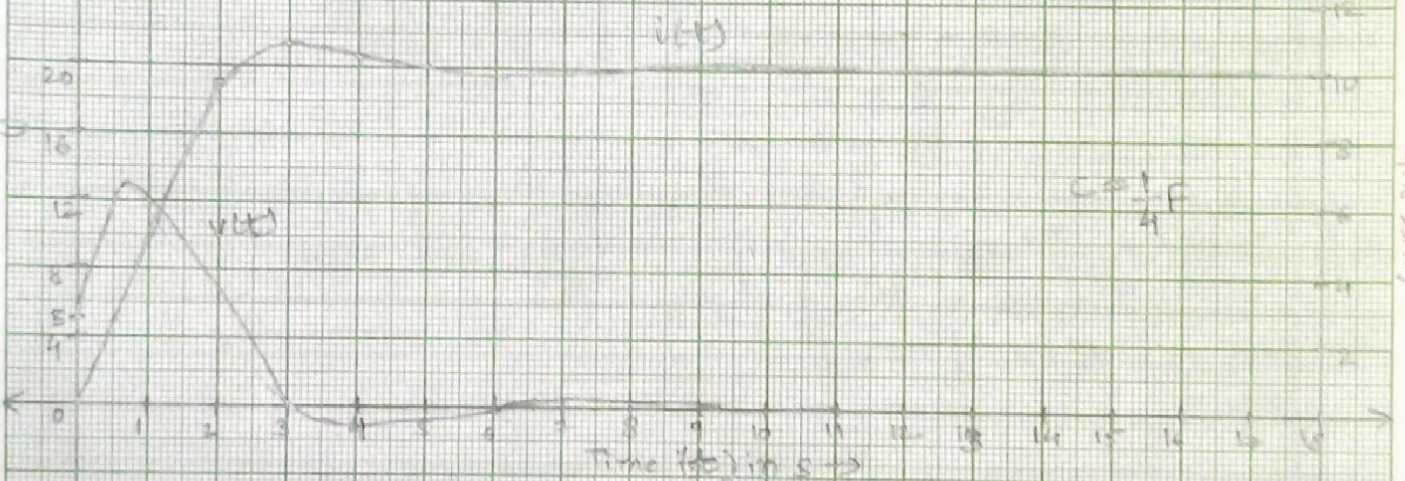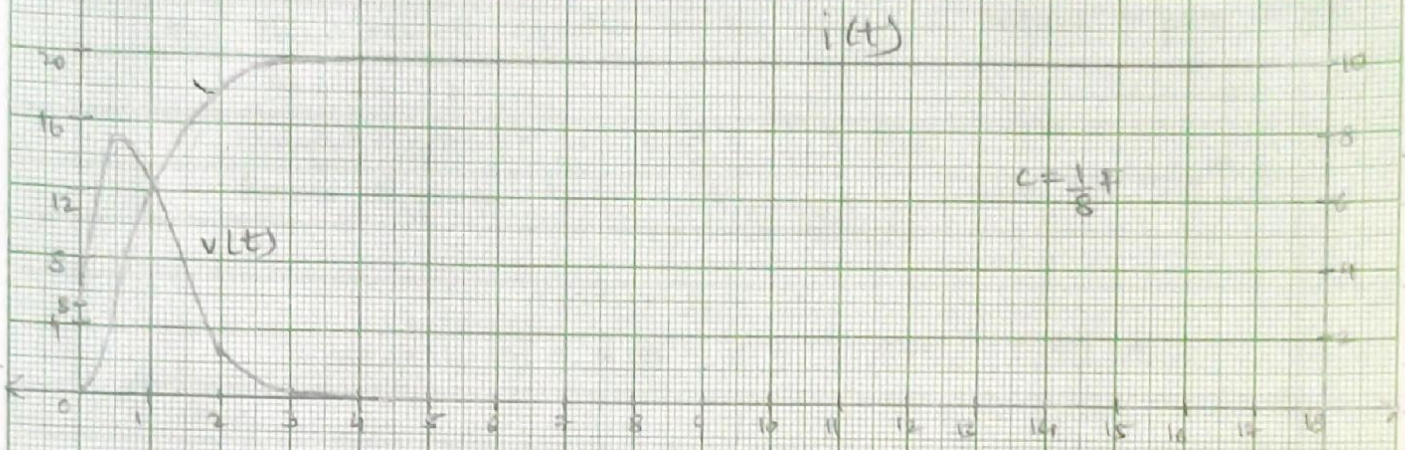
Voltage across Capacitor $V(t)$ in V \rightarrow



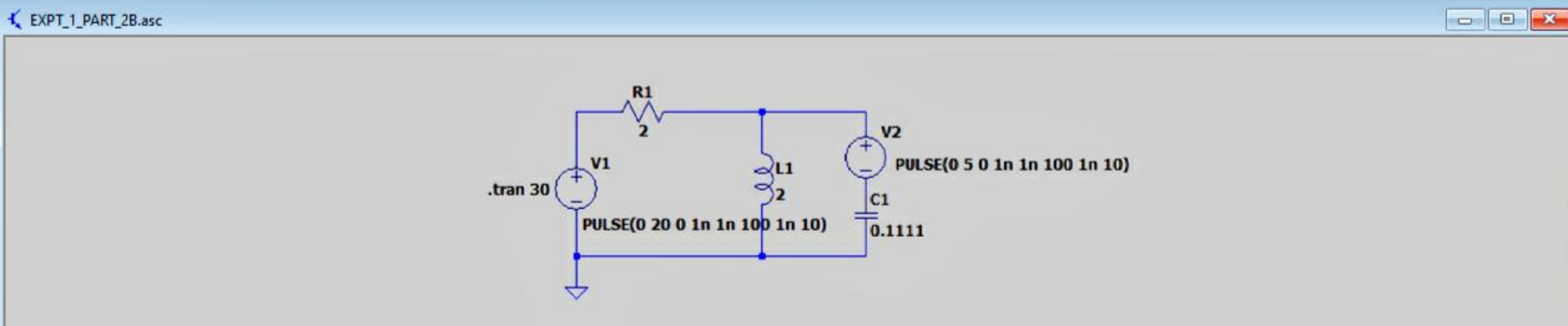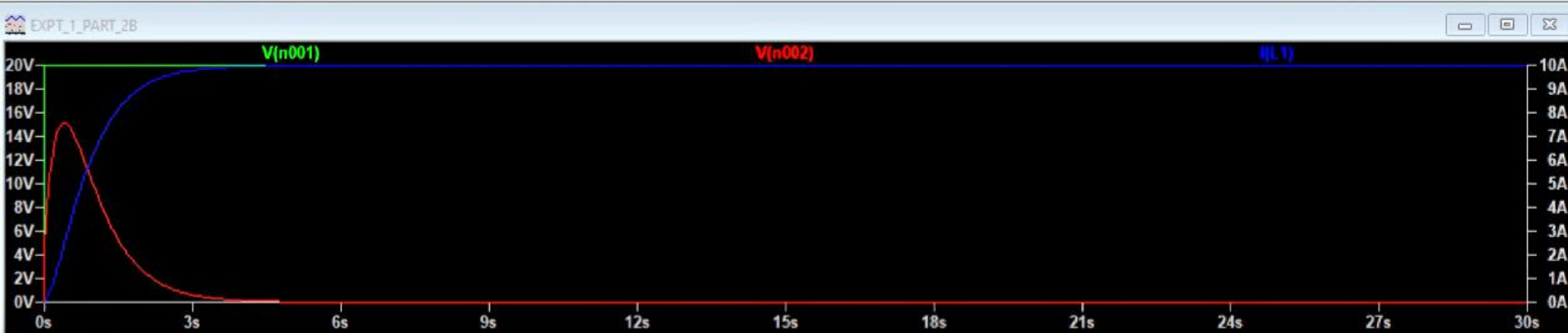Current across Inductor $i(t)$ in A \rightarrow



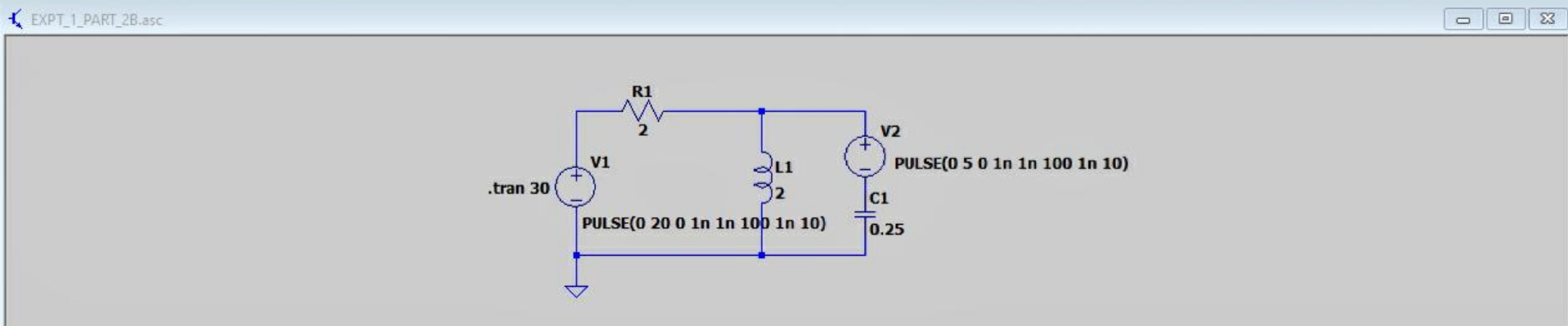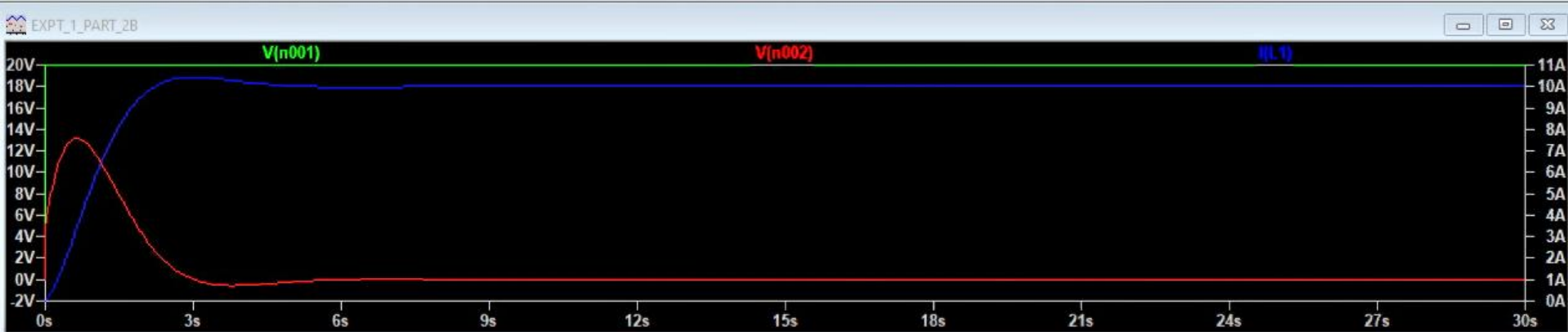

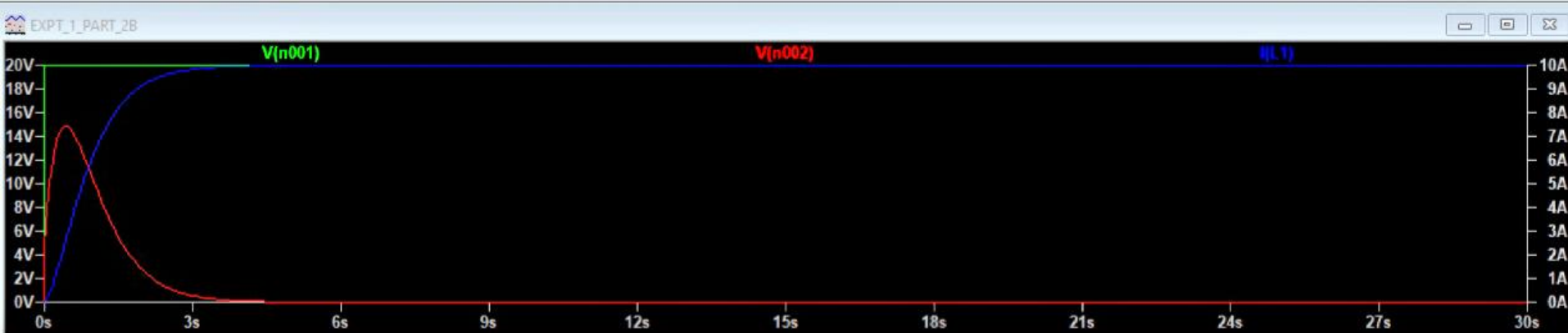

EXPT_1_PART_2B.asc

