

Experiment 3 Part 1

Objective : Experimental verification of Fourier Coefficients of a Square wave signal using Passive Network

Theory : Any periodic signal can be broken down into sine and cosine waves, in the form of

$$x(t) = a_0 + (a_1 \cos \omega t + a_2 \cos 2\omega t + a_3 \cos 3\omega t \dots) \\ + (b_1 \sin \omega t + b_2 \sin 2\omega t + b_3 \sin 3\omega t \dots)$$

where $x(t)$ is the periodic signal and ω is the fundamental angular frequency.

$$\Rightarrow x(t) = a_0 + (a_1 \cos \omega t + b_1 \sin \omega t) + (a_2 \cos 2\omega t + b_2 \sin 2\omega t \dots) \\ = a_0 + \sqrt{a_1^2 + b_1^2} \left[\frac{a_1 \cos \omega t + b_1 \sin \omega t}{\sqrt{a_1^2 + b_1^2}} \right] \\ + \sqrt{a_2^2 + b_2^2} \left[\frac{a_2 \cos 2\omega t + b_2 \sin 2\omega t}{\sqrt{a_2^2 + b_2^2}} \right] \dots \\ = a_0 + \sqrt{a_1^2 + b_1^2} \sin(\omega t + \phi_1) + \sqrt{a_2^2 + b_2^2} \sin(2\omega t + \phi_2) \dots$$

$$\text{where } \tan \phi_n = \frac{a_n}{b_n}$$

$$\therefore x(t) = a_0 + \sum_{n=1}^{\infty} \sqrt{a_n^2 + b_n^2} \sin(n\omega t + \phi_n)$$

Equipment (Simulink Blocks) Needed :

- Controlled Voltage Source
- Signal Generator
- 2 x Voltage Measurement
- 2 x Scope
- Series RLC Branch (Made into Resistor)
- Series RLC Branch (Made into Inductor)
- Series RLC Branch (Made into Capacitor)
- 2 x ~~Fourier~~ Fourier (one for Input, other for Output)
- Add


Practicals without load

19CS10039


8/1/23

Carry

KAUSHAL
BANTHIA

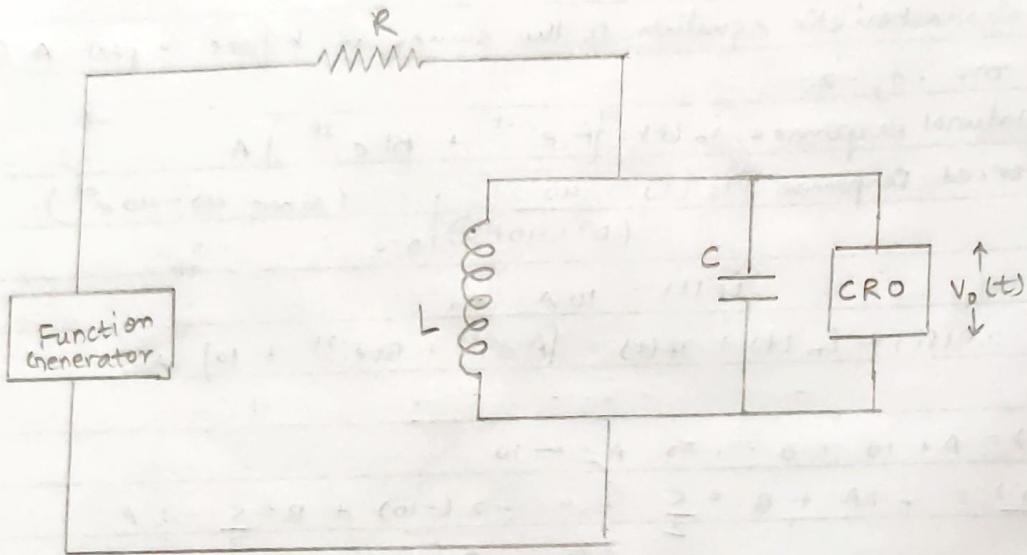
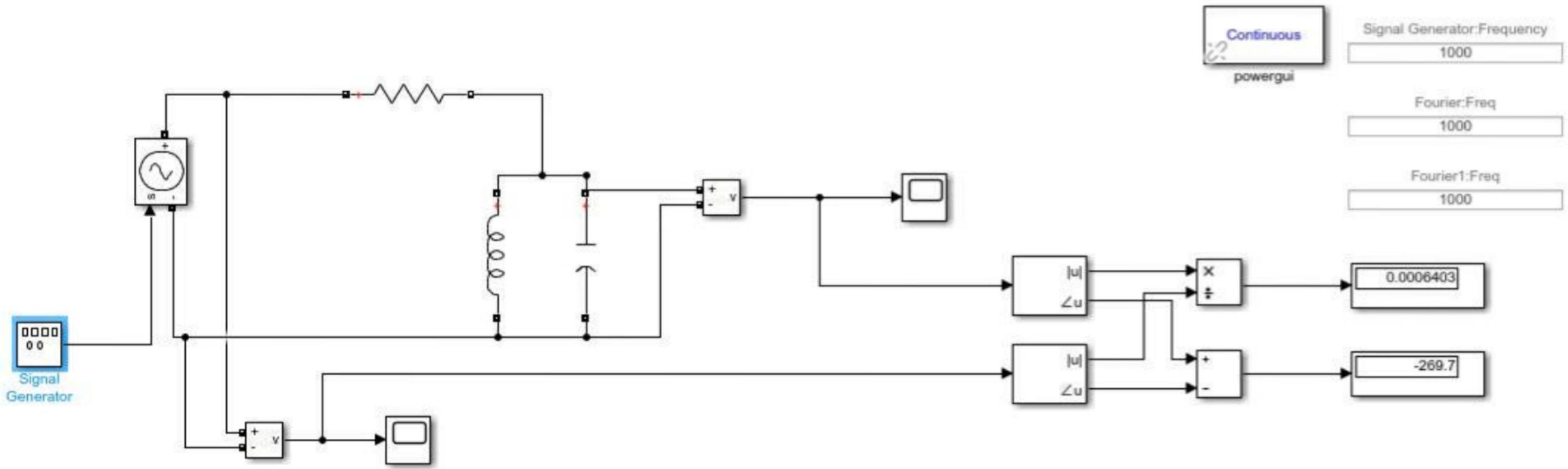
$$V_o(t) = 300 \sin(100\pi t + 45^\circ)$$



- Divide
- 2x Display
- Powergui (continuous)
- 3x Edit


Part I

Simulink Procedure for running the experiment:

- Right Click in the Background and choose Model Configuration Parameters. In the menu that opens, we choose the solver that has the name 'ode23t (mod. stiff / Trapezoidal)'
- Set the Stop time to 5s at the top of the window
- Then click Run. after taking 3V and 100Hz, in ~~the~~ signal generator
- Vary frequency after each run to obtain the table below.

Observation Table: for $V_{in} = 3V$ (Amplitude) for sine wave

frequency (f) in Hz	V_{out} (in V)	Gain	
100	1.895×10^{-4}	6.317×10^{-5}	$R = 100 k\Omega$
1000	1.968×10^{-3}	6.56×10^{-4}	$L = 10 mH$
2000	4.437×10^{-3}	1.479×10^{-3}	$C = 100 nF$
3000	8.898×10^{-3}	2.966×10^{-3}	
4000	2.1×10^{-2}	7×10^{-3}	
5000	1.283	4.276×10^{-1}	
5016	2.996	9.985×10^{-1}	
5017	3.003	1.001	
5018	2.985	9.883×10^{-1}	
5030	1.529	5.098×10^{-1}	
7500	1.137×10^{-2}	3.789×10^{-3}	
10000	6.333×10^{-3}	2.111×10^{-3}	
15000	3.549×10^{-3}	1.183×10^{-3}	
30000	1.629×10^{-3}	5.431×10^{-4}	
70000	7.125×10^{-4}	2.375×10^{-4}	
100000	4.749×10^{-4}	1.583×10^{-4}	

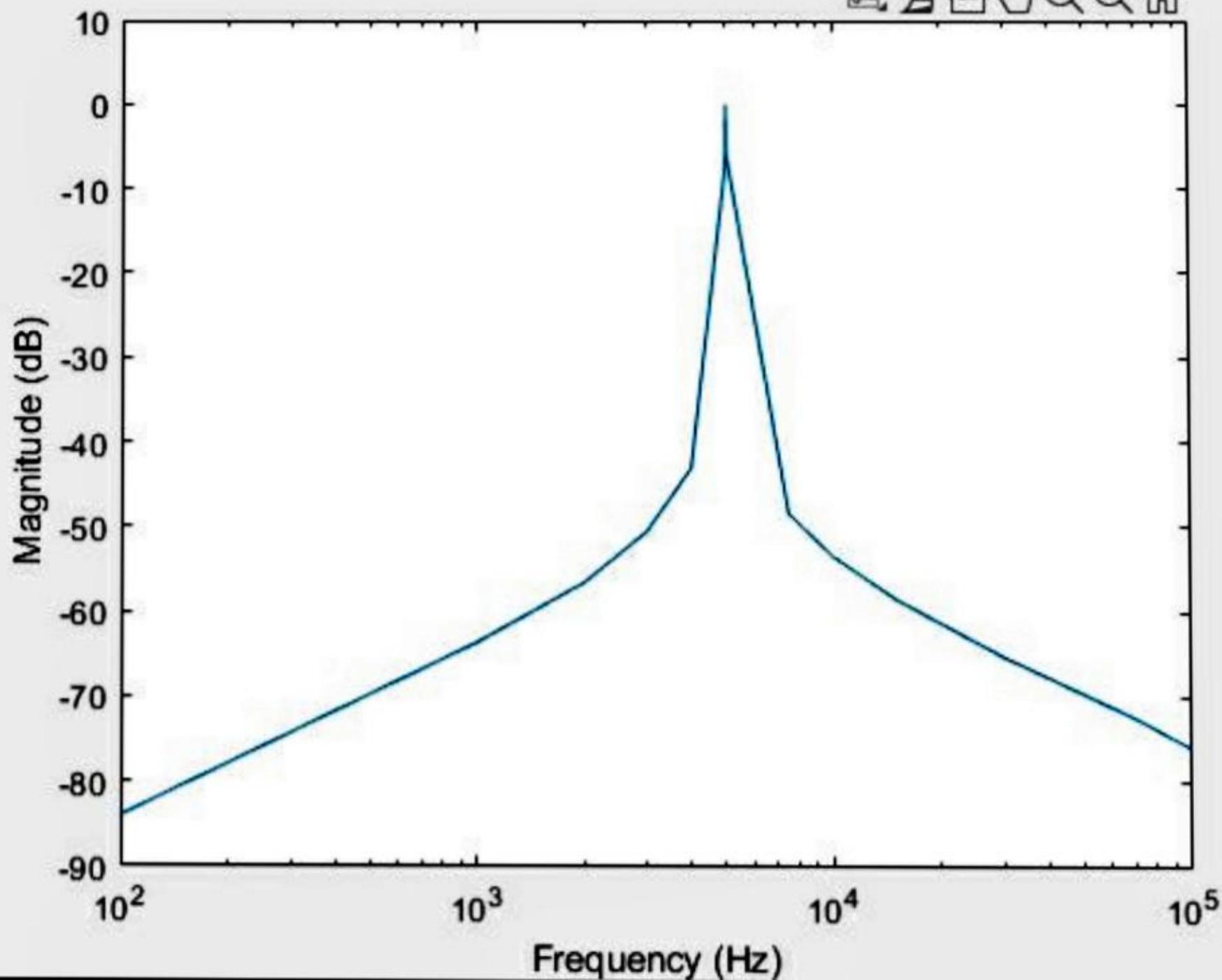

Converting the circuit into Laplace domain, we get

$$R \rightarrow R$$

$$L \rightarrow LS$$

$$C \rightarrow \frac{1}{CS}$$

$$\therefore \text{Now } Y(s) = G(s) \cdot X(s)$$

↓
Transfer Function

$$\Rightarrow G(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

$$G(s) = I \cdot \frac{LS \cdot \frac{1}{CS}}{[LS + \frac{1}{CS}]} \cdot \frac{1}{V_{in}(s)}$$

$$G(s) = \frac{V_{in}(s)}{\left[R + \frac{LS \cdot \frac{1}{CS}}{LS + \frac{1}{CS}} \right]} \cdot \left[\frac{LS \cdot \frac{1}{CS}}{LS + \frac{1}{CS}} \right] \cdot \frac{1}{V_{in}(s)}$$

$$\therefore G(s) = \frac{\frac{L}{C}}{\frac{LCS^2 + 1}{CS}} \cdot \frac{1}{R + \frac{\frac{L}{C}}{\frac{LCS^2 + 1}{CS}}} \\ = \frac{LS}{LCS^2 + 1} \cdot \frac{1}{R + \frac{LS}{LCS^2 + 1}}$$


$$= \frac{1}{1 + \frac{R}{LS} (LCS^2 + 1)}$$

$$G(s) = \frac{LS}{LS + R(LCS^2 + 1)} = \frac{10 \times 10^{-3} s}{10 \times 10^{-3} s + 100 \times 10^3 (10 \times 10^{-3} \times 100 \times 10^{-9} s^2 + 1)}$$

$$G(s) = \frac{10^{-2} s}{10^{-2} s + 10^5 (10^{-9} s^2 + 1)} = \frac{s}{s + 10^4 (10^{-9} s^2 + 1)}$$

$$G(s) = \frac{s}{s + \frac{100 s^2}{100} + 10^7}$$

Bode Diagram

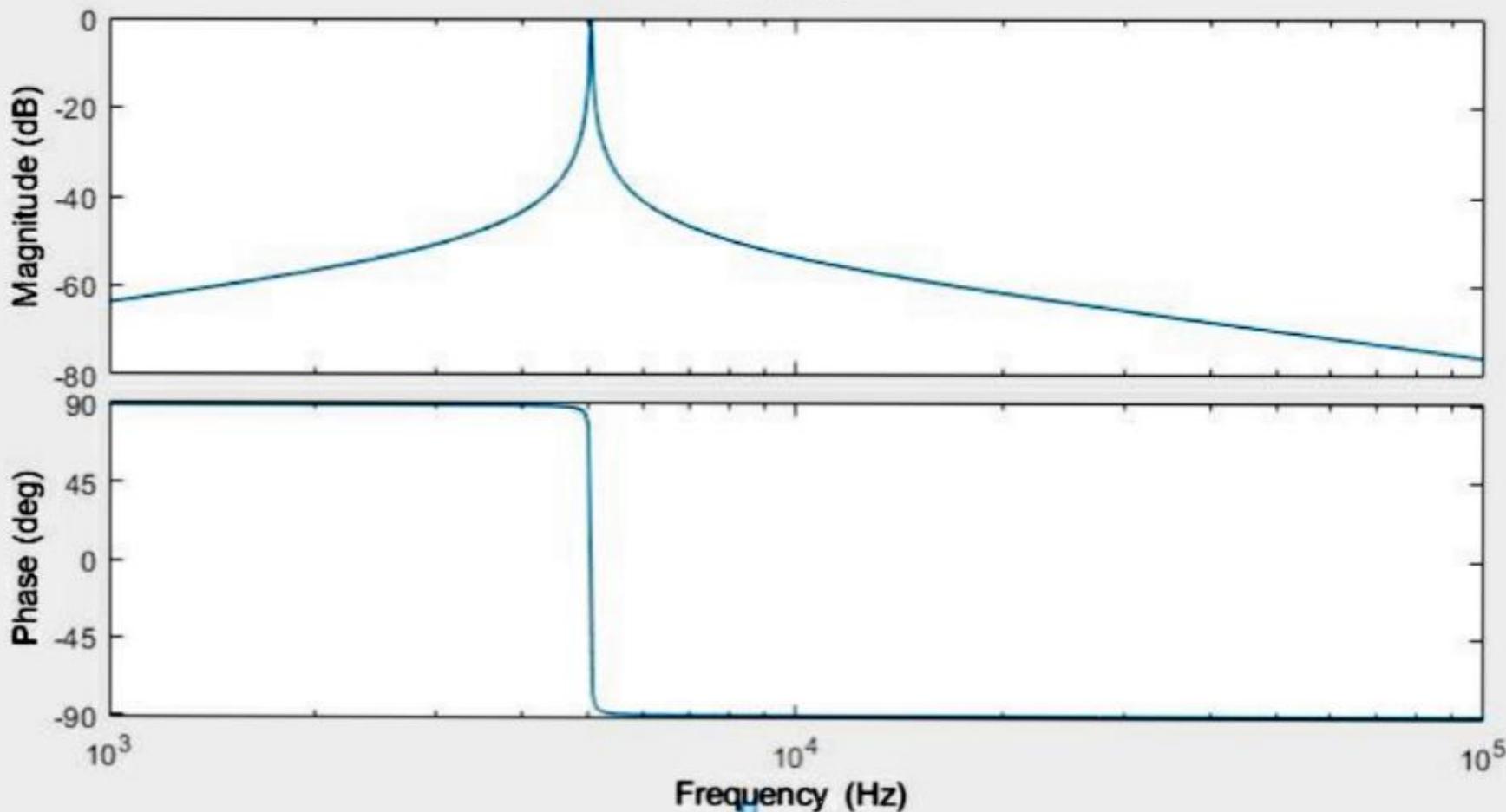

Discussion: The observational peak of the magnitude graph (in dB) comes at 5017 Hz, whereas, the theoretical peak comes at 5033Hz.

$$\text{Thus, the error percentage} = \left| \frac{5033 - 5017}{5033} \right| \times 100\% \\ = [0.318\%]$$

Using this part, we found the fundamental frequency.

Part II

Simulink Procedure for running the experiment:

- Click Run
- Vary frequency after each taking 3V and 5017 Hz square wave in signal generator.
- Vary frequency by 1Hz each time. (fine tuning)

Observation Table: for $V_{in} = 3V$ for square wave

frequency (f) in Hz	V_{out} (in V)	$Gain$	$R = 100 \text{ k } \Omega$
5017	3.530	1.177	$L = 10 \text{ mH}$
5018	3.574	1.191	$C = 100 \text{ nF}$
5019	3.631	1.210	
5020	3.758	1.252	
5021	3.82	1.273	
5022	3.815	1.272	
5023	3.764	1.255	

V_{out} and Gain are maximum for $f = 5021 \text{ Hz}$ (After fine tuning)

Thus, $V_{out} = 3.82 \text{ V}$ is the fundamental fourier series coefficient.

Since the square wave signal is an odd function, thus we have all $a_i \neq 0$ ($i = 0, 1, 2, 3, \dots$)

Thus, this $V_{out} = 3.82 \text{ V}$ is the term b_1

$$\therefore b_1, \text{ observed} = 3.82 \text{ V}$$

$$\begin{aligned}
 \text{Now, } b_1, \text{ theoretical} &= \frac{2}{T} \int_0^T x(t) \sin(\omega t) dt \\
 &= 2(5021) \int_{\pi/2}^{\pi/2} (-3) (\sin \omega [(2\pi)(5021)t]) dt \\
 &\quad + \\
 &2(5021) \int_{\pi/2}^{\pi/2} (-3) (\sin [(2\pi)(5021)t]) dt \\
 &= 3.8197 V.
 \end{aligned}$$

Discussion: The observed b_1 is 3.82 V, while the theoretical b_1 is 3.8197 V.

$$\begin{aligned}
 \therefore \text{error percentage} &= \frac{|3.8197 - 3.82|}{3.8197} \times 100\% \\
 &= 0.00785\%
 \end{aligned}$$

This percentage is very small and can be ignored as approximation error.

In this part, we found the fundamental fourier coefficient of $x(t)$.

Part III

Simulink Procedure for running the experiment

- Change frequency to $\frac{1}{3}$ rd of 5021 Hz \approx 1674 Hz, and voltage = 3V Square wave in signal generator
- Vary frequency by 1Hz each time (fine tunings)
- Click Run

Observation Table (for Vin = 3V for square wave)

Frequency (f) in Hz	Vout (in V)	Gain	
1.672	1.185	0.395	$R = 100k\Omega$
1.673	1.258	0.419	$L = 10mH$
1.674	1.281	0.427	$C = 100nF$
1.675	1.229	0.409	
1.676	0.8779	0.293	

Brain and V_{out} are maximum for $f = 1674 \text{ Hz}$ (After fine tuning)
 Thus, $V_{out} = 1.281 \text{ V}$ is the 3rd Harmonic Fourier Series Coefficient
 $\therefore b_3, \text{ observed} = 1.281 \text{ V.}$

$$\begin{aligned} \text{Now, } b_3, \text{ theoretical} &= \frac{2}{T} \int_0^{T/2} x(t) \sin(3\omega t) dt \\ &= 2(5021) \int_0^{T/2} 3 \sin(3 \cdot 2\pi \cdot 5021 t) dt \\ &\quad + \\ &2(5021) \int_{T/2}^T (-3) \sin(3 \cdot 2\pi \cdot 5021 t) dt \\ &= 1.2732 \text{ V.} \end{aligned}$$

Discussion: The observed b_3 is 1.281 V and the theoretical b_3 is 1.2732 V. \therefore The percentage error is $\frac{|1.281 - 1.2732| \times 100}{1.2732} = 0.61\%$

This is a small error which may be caused due to division,
~~since we use~~ since we use $f = 1674 \text{ Hz}$, which is not exactly ~~5021~~ 5021 Hz divided by 3.

Simulink Procedure for running the experiment:

- change frequency to $\frac{1}{5}$ th of $5021 \text{ Hz} \approx 1004 \text{ Hz}$. and voltage = 3 V square wave in signal generator.
- vary frequency by 1 Hz each time (fine tuning)
- Click Run.

Observation Table: for $V_{in} = 3V$, for Square wave.

frequency (f) in Hz	V_{out} (in V)	Chain
1002	0.463	0.154
1003	0.696	0.232
1004	0.789	0.256
1005	0.740	0.247
1006	0.393	0.131

Chain and V_{out} are maximum for $f = 1004 \text{ Hz}$ (After fine tuning).
 Thus, $V_{out} = 0.789 \text{ V}$ is the 5th Harmonic Fourier series coefficient.
 $\therefore b_5, \text{ observed} = 0.789 \text{ V.}$

$$\begin{aligned} \text{Now } b_5, \text{ theoretical} &= \frac{2}{T} \int_0^T n(t) \sin(5\omega t) dt \\ &= \frac{2}{T} \int_0^{T/2} 3 \sin(5 \cdot 2\pi \cdot 5021 t) dt \\ &\quad + \\ &2(5021) \int_{T/2}^T (-3) \sin(5 \cdot 2\pi \cdot 5021 t) dt \\ &= 0.7839 \text{ V.} \end{aligned}$$

Discussion: The observed b_5 is 0.789 V while the theoretical b_5 is 0.7839 . \therefore Percentage error = $\frac{|0.789 - 0.7839|}{0.789} \times 100\%$

$$= 0.66\%$$

This is a small error which may be caused due to division, since we use $f = 1004 \text{ Hz}$, which is not exactly 5021 Hz divided by 5.

Discussion: In this experiment, we found out the different fourier series coefficients of the input signal.

Here the $a_0, a_1, a_2, a_3 \dots$ terms were 0 since the input signal was an odd signal.

Using this experiment, we can find the different components of any periodic signal, if we keep on going for all the harmonics. After that, we can break the signal into sines and cosines, which can further be broken down into summations of e^{jt} and e^{-jt} .

Now, we know that e^{st} is an eigen function of any LTI system. Thus, when this signal is input in any ~~LTI~~ LTI system, we get an output of $H(s) \cdot e^{st}$ where $H(s)$ is the transfer function of that system. Now this $H(s)$ is a constant w.r.t. time t .

Thus, when e^{st} is input in any ~~LTI~~ LTI system, we get a ~~fund~~ signal of the similar.

This information can also be used in the following way →

- Given a certain response.
- Break into its corresponding sines and cosines and then e^{st} .
- Find each exponential's input by getting $\frac{e^{st}}{H(s)}$.
- sum all these inputs.
- Get the input signal for the output signal.

Thus, if we have the ability to breakdown any signal into its corresponding sines and cosines, and ~~corr~~ thus, e^{st} , we can then find the response for any input and also the input for any response for any LTI system, given its transfer function..

This experiment provides us with this ability to breakdown periodic signals into their corresponding sines and cosines and thus e^{st} .