

Experiment 3 Part 2

Objective: To find the frequency of an RLC circuit for different values of resistance (and thus zeta)

Theory: For the given series RLC circuit, we can obtain the same circuit in Laplace domain by making $R \rightarrow R$, $L \rightarrow LS$, $C \rightarrow \frac{1}{Cs}$.

Then, we have $d\{V_o(t)\} = I \cdot \frac{1}{Cs}$

$$d\{V_o(t)\} = d\{V_{in}(t)\} \cdot \frac{1}{R + LS + \frac{1}{Cs}}$$

$$\Rightarrow \frac{d\{V_o(t)\}}{d\{V_{in}(t)\}} = \frac{1}{Rcs + Lcs^2 + 1}$$

$$\text{Now } Y(s) = H(s) \cdot X(s)$$

where $Y(s)$ is Output, $X(s)$ is Input and $H(s)$ is transfer function

$$\therefore H(s) = \frac{Y(s)}{X(s)}$$

$$\therefore \text{Our } H(s) = \frac{1}{Lcs^2 + Rcs + 1} \quad \text{---(1)}$$

Now, the standard Laplace domain transfer function is given by,

$$H(s) = \frac{1}{(\frac{1}{\omega_n^2})s^2 + (\frac{2\zeta_p}{\omega_n})s + 1} \quad \text{(for series RLC)} \quad \text{---(2)}$$

\therefore On comparing (1) and (2), we get,

$$\omega_n = \sqrt{\frac{1}{LC}}$$

$$\frac{2\zeta_p}{\omega_n} = RC \Rightarrow \zeta_p = RC \frac{\omega_n}{2} = \frac{R}{2} C \cdot \frac{1}{\sqrt{LC}} = \frac{R}{2} \sqrt{\frac{C}{L}}$$


$$\Rightarrow R = 2 \zeta_p \sqrt{\frac{L}{C}}, \text{ where } L = 0.1 \text{ H and } C = 0.1 \mu\text{F}$$


$$\therefore R = 2 \zeta_p \sqrt{\frac{0.1}{0.1 \times 10^{-6}}} = 2 \zeta_p \times 10^3$$

E0012351

KAUSHAL
BANTHIA

19CS10039

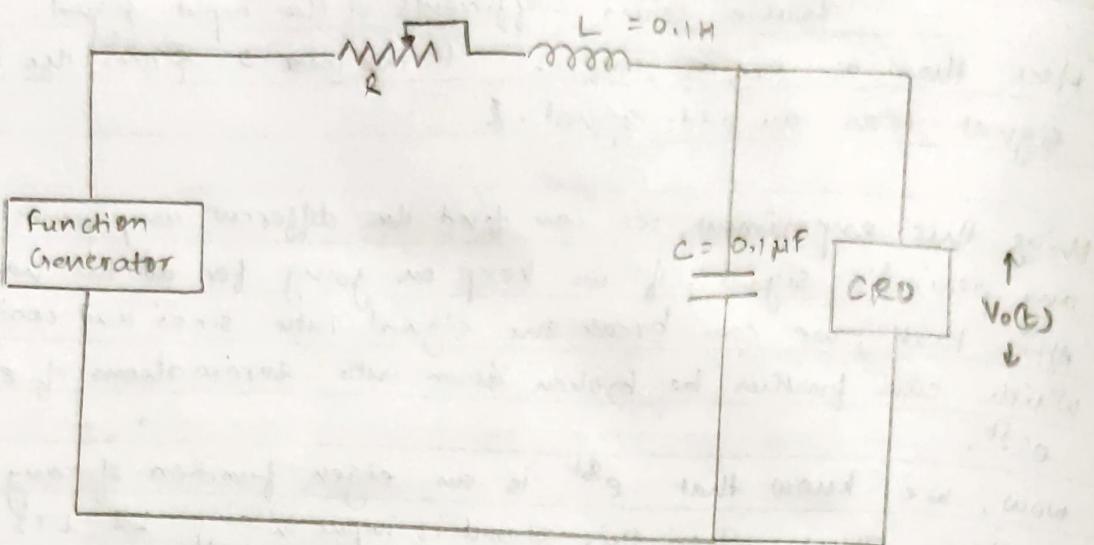Kaushal

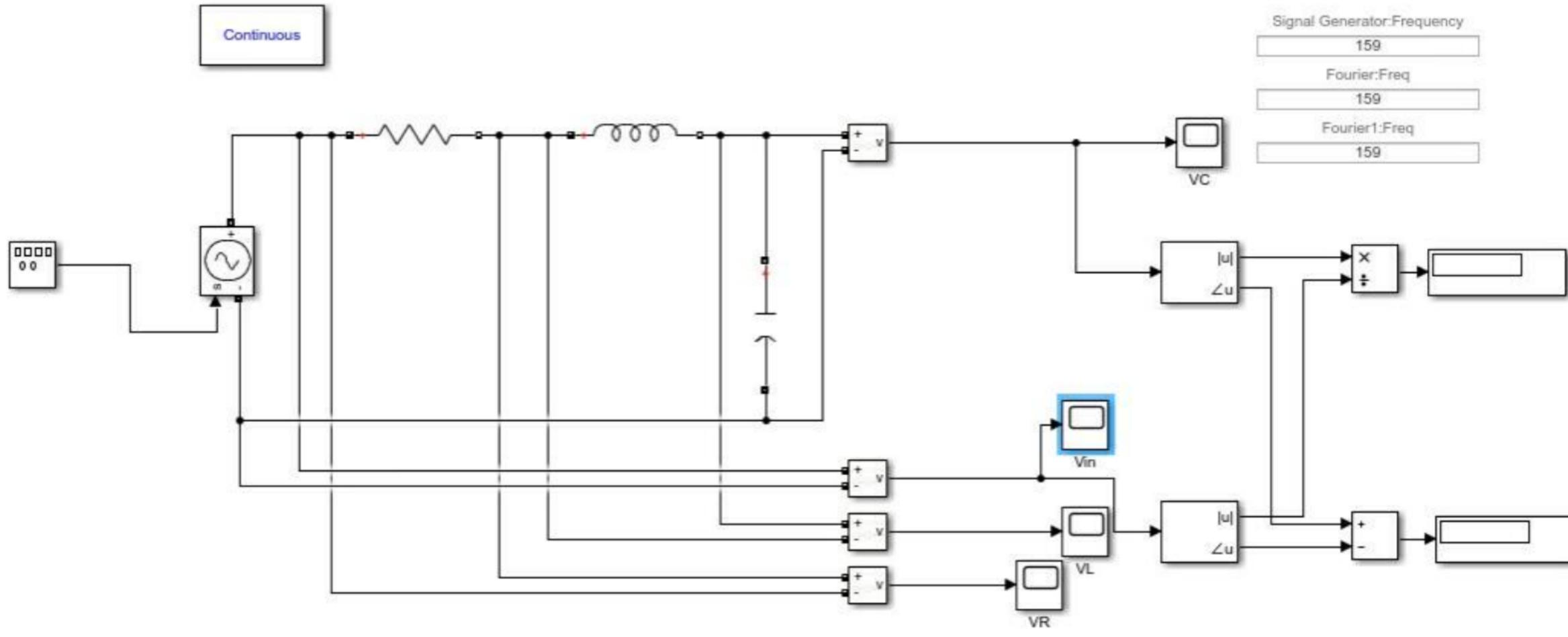

$$\therefore R = 2000 \frac{V_p}{\omega} \Omega$$

Equipment (Simulink Blocks) Needed :

- Controlled Voltage Source
- Signal Generator
- Series RLC Branch (Made into Resistor)
- Series RLC Branch (Made into Inductor)
- Series RLC Branch (Made into capacitor)
- Powergui (Continuous)
- 4x Voltage Measurement
- UX Scope
- 2x Fourier
- Add
- Divide
- 2x Display
- 3x Edit

Simulink Procedure for Running the experiment :


- Change the solver to ode23t this time.
- Set Amplitude to 3V in the signal generator (Sine Wave)
- Set ~~R~~ L = 0.1 mH and C = 0.1 μF and then vary R according to zeta values.
- Click Run and measure Voltage across R, C, L and then find Vout / Vin and Phase.
- Perform this experiment for different frequencies to obtain a range of values.
- Plot the magnitude response
- Plot the phase response.


Observation Table:

$$(i) \frac{V_o}{V_i} = 0.2 \Rightarrow R = 2000 \times 0.2 = 400 \Omega$$


for input (Vin) of $\pm 3V$ Amplitude Sine Wave,

frequency (f) in Hz	Vc (in V)	VL (in V)	VR (in V)	Gain (Vc/Vin)	Phase (Degrees)
150	3.025	0.030	0.121	1.010	-2.232
250	3.070	0.078	0.193	1.024	-3.612
300	3.101	0.110	0.234	1.034	-4.378
400	3.183	0.201	0.320	1.062	-6.050
1000	4.586	1.817	1.154	1.529	-22.500
1420	7.314	5.843	2.615	2.441	-60.408
1441	7.428	6.114	2.696	2.480	-63.721
1460	7.518	6.348	2.764	2.509	-66.847
1500	7.632	6.810	2.884	2.549	-73.730
2000	3.878	6.156	1.954	1.294	-139.120
5000	0.332	3.303	0.419	0.111	-171.480
7500	0.140	3.128	0.264	0.047	-174.310
10000	0.077	3.071	0.195	0.026	-175.490
12000	0.053	3.043	0.161	0.018	-176.390

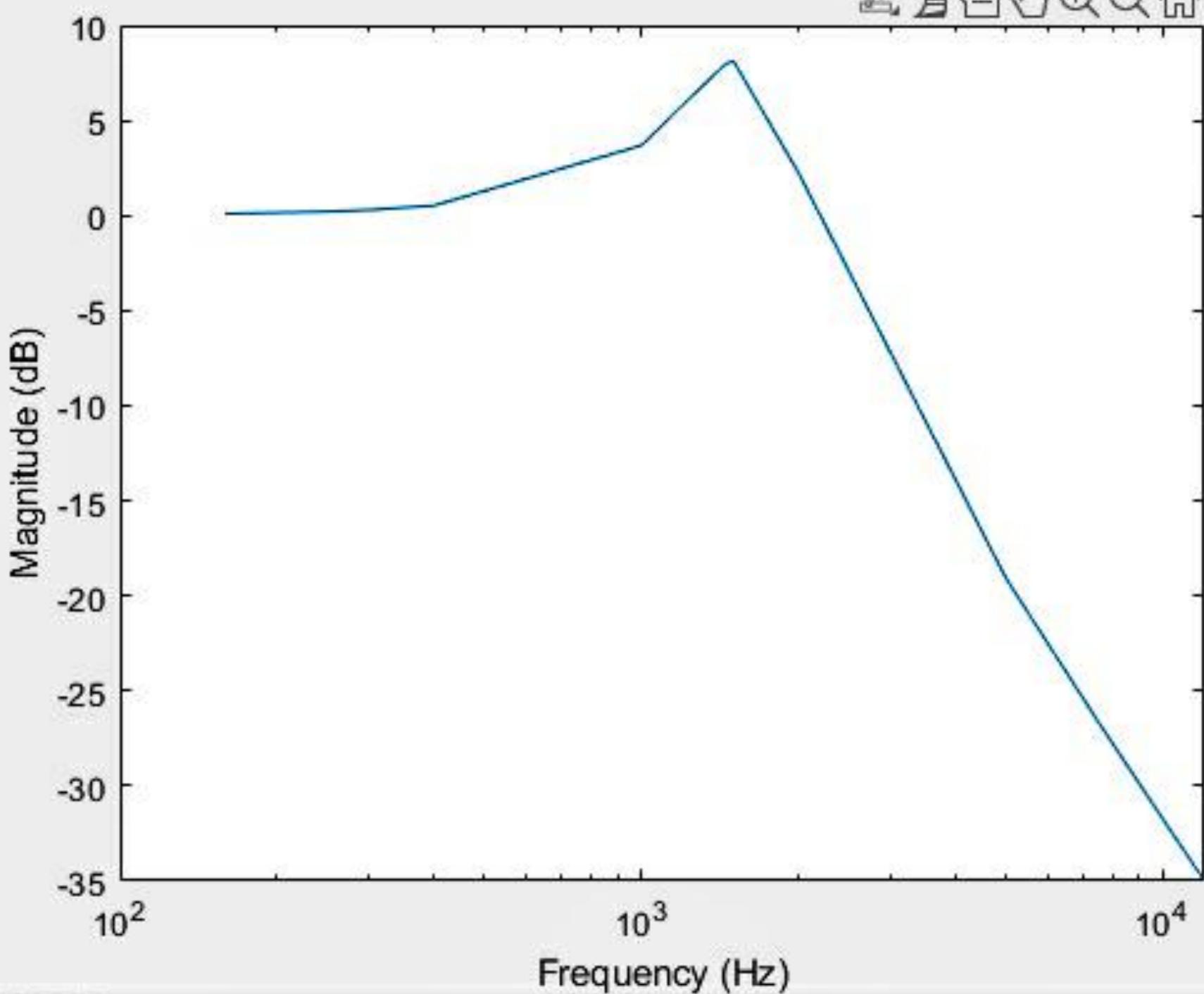

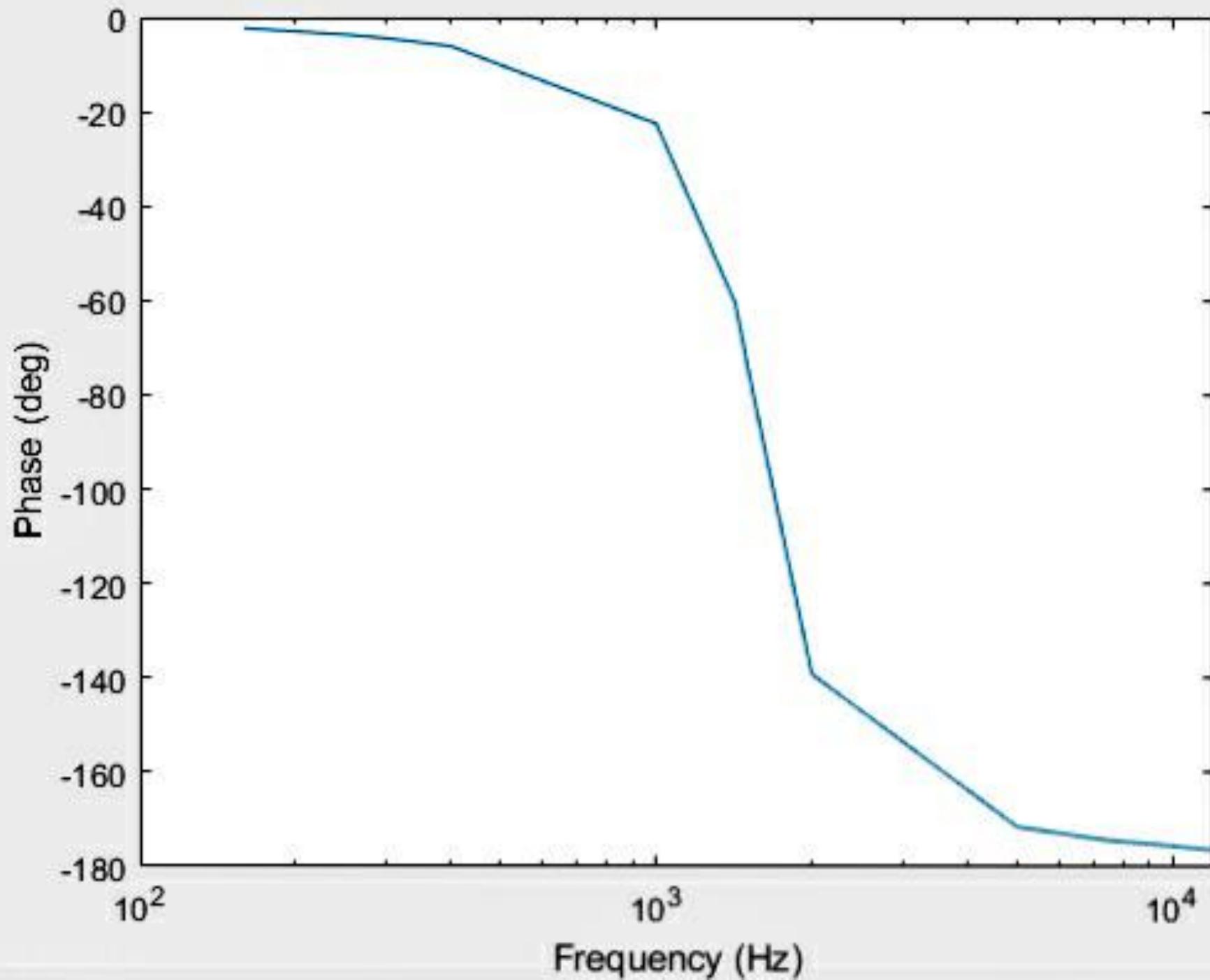

Bode Diagram

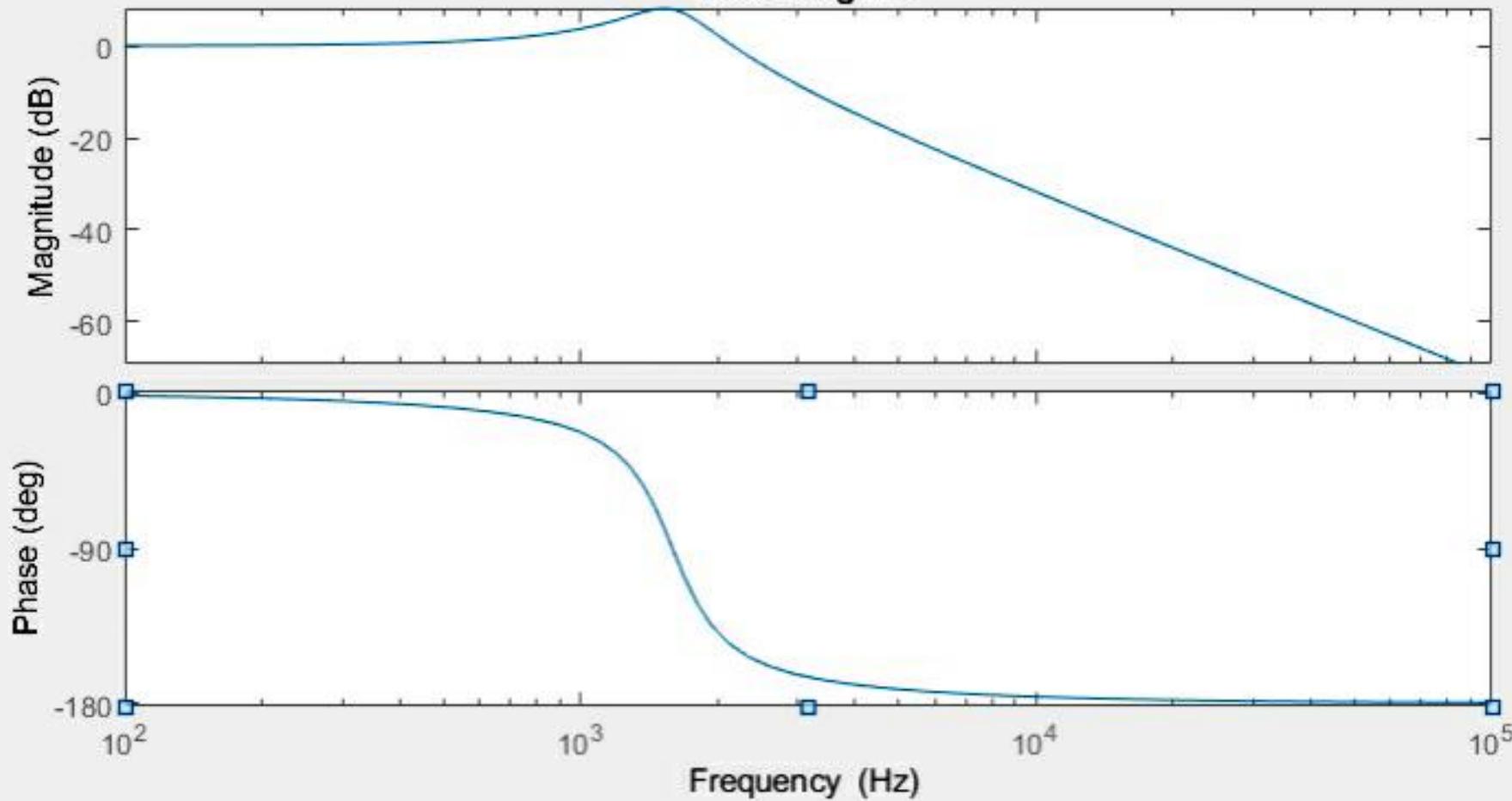



(ii)

$$\xi = 0.7 \Rightarrow R = 2000 \pi \cdot 0.7 = 1400 \Omega$$


For input = 3V (Amplitude) Sine wave.
(V_{in})

Frequency (f) in Hz	V _c (in V)	V _L (in V)	V _R (in V)	Gain (V _c / V _{in})	Phase (Degree)
159	2.995	0.030	0.419	0.998	-7.950
250	2.992	0.074	0.661	1.000	-12.644
300	3.000	0.107	0.793	0.998	-15.224
400	2.990	0.190	1.054	0.997	-20.500
1000	2.809	1.112	2.474	0.938	-55.420
1420	2.367	1.891	2.962	0.790	-80.631
1441	2.339	1.925	2.977	0.781	-81.846
1460	2.315	1.955	2.978	0.772	-82.842
1500	2.261	2.017	2.990	0.755	-85.010
2000	1.614	2.561	2.846	0.538	-108.120
5000	0.301	2.991	1.328	0.101	-153.220
7500	0.134	2.999	0.888	0.045	-162.000
10000	0.075	3.001	0.666	0.025	-166.610
12000	0.052	3.001	0.555	0.018	-168.690

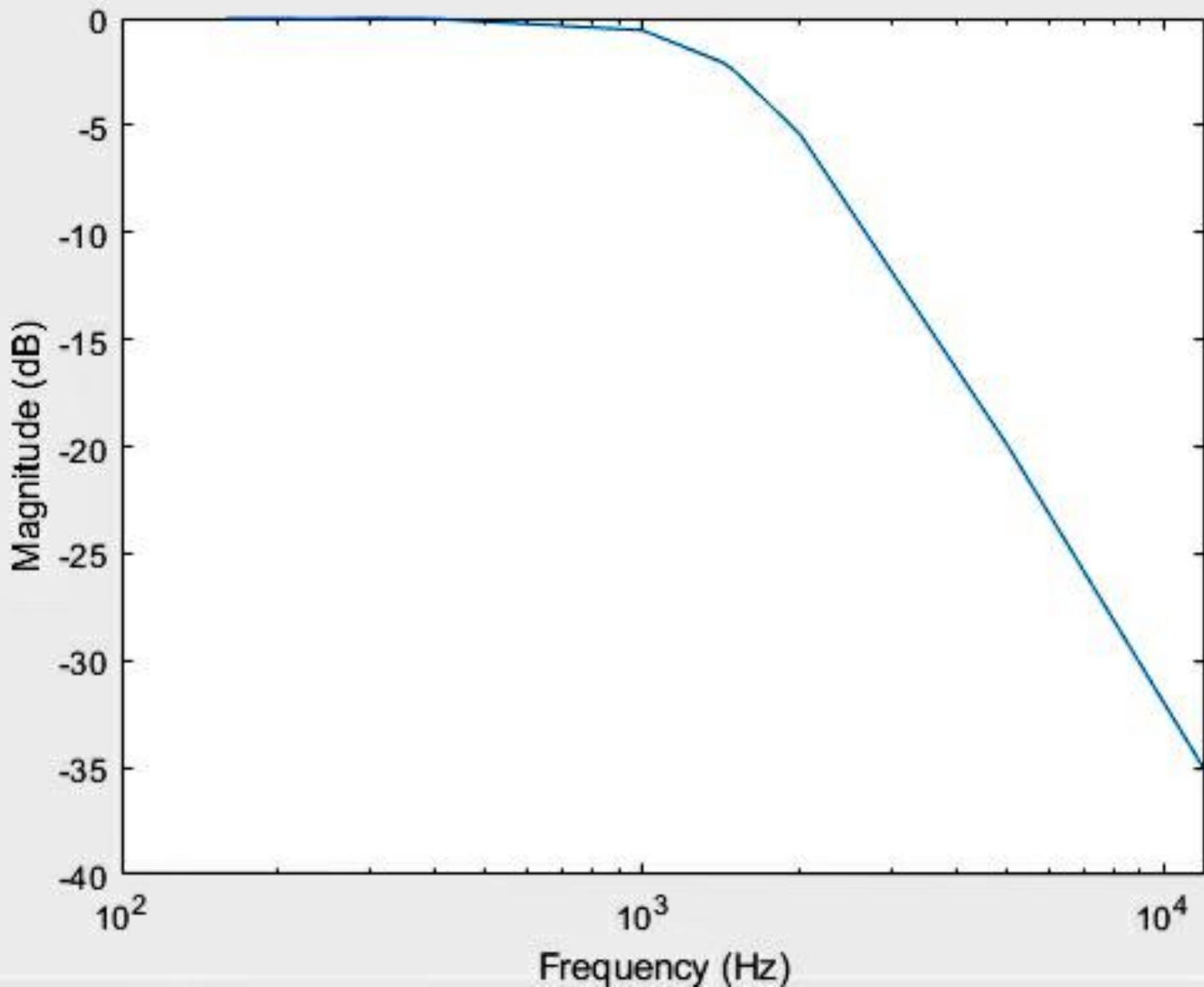

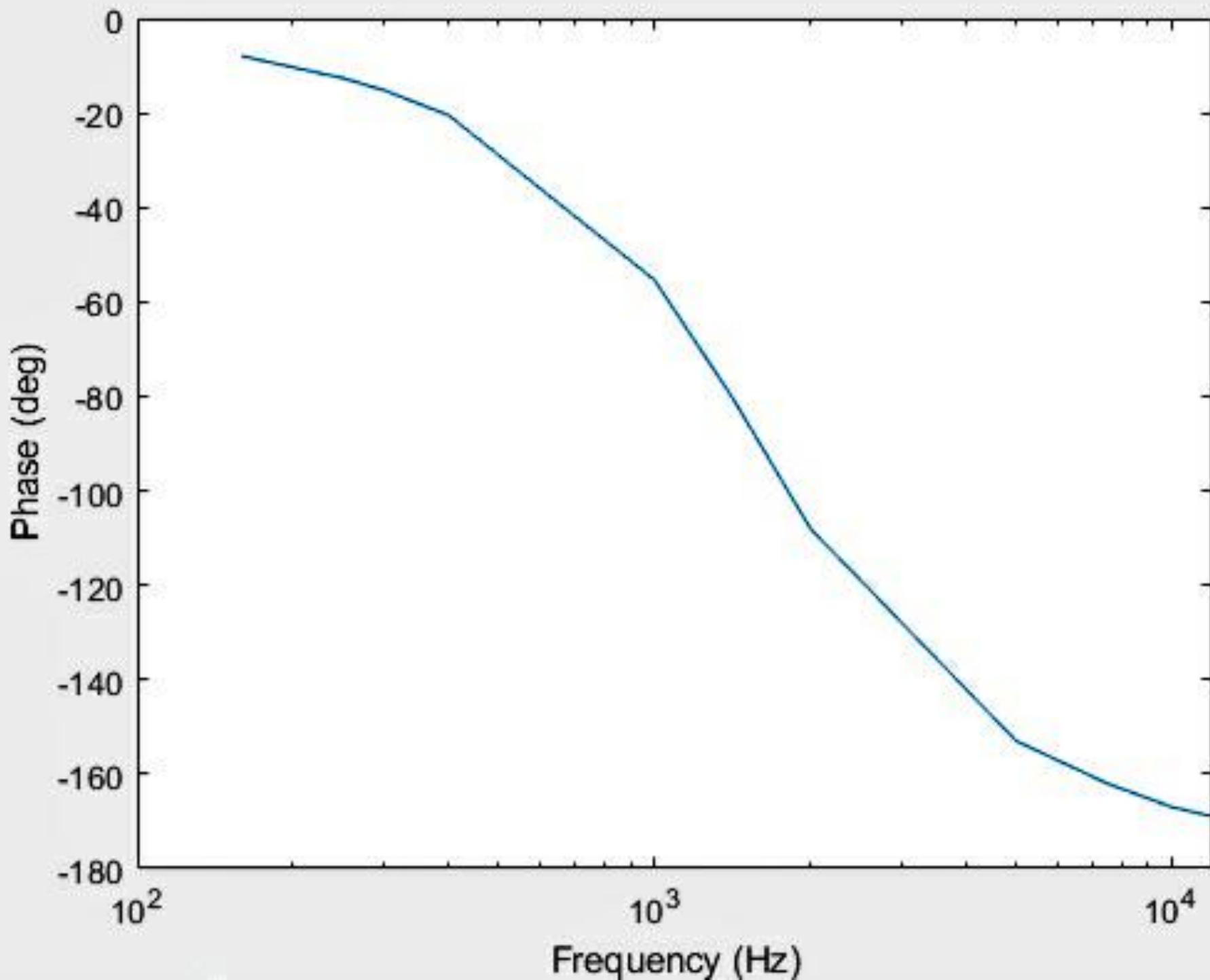

Bode Diagram

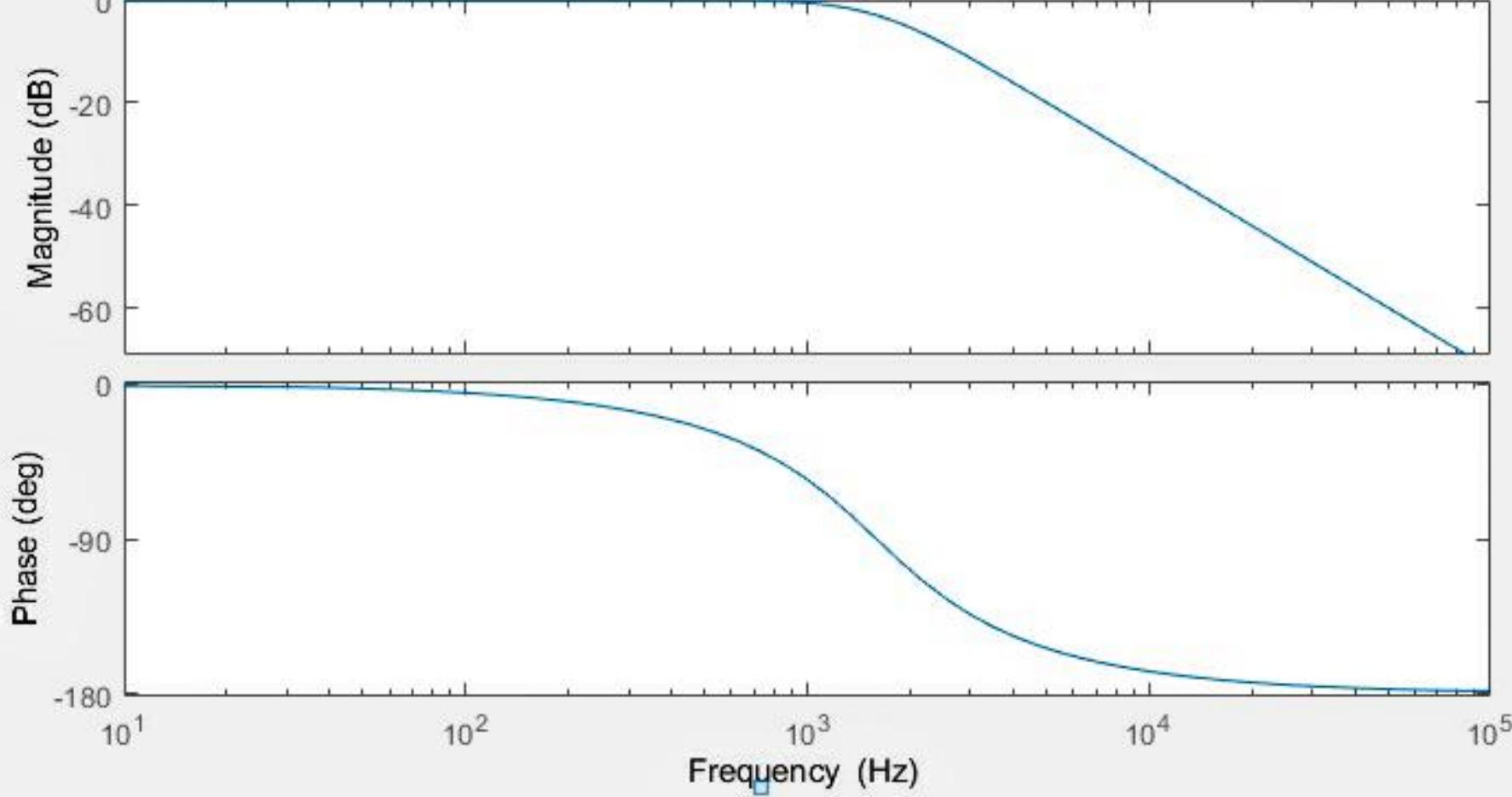



~~Done by~~

$$(ii) \quad \xi_f = 0.95 \Rightarrow R = 2000 \times 0.95 = 1900 \Omega$$


for input (V_{in}) = 3V (Amplitude) as sine wave.

frequency (f) in Hz	V_C (in V)	V_L (in V)	V_R (in V)	Gain (V_C/V_{in})	Phase (Degree)
150	2.970	0.030	0.585	0.993	-10.790
250	2.936	0.073	0.877	0.981	-17.010
300	2.913	0.104	1.046	0.973	-20.270
400	2.852	0.181	1.364	0.951	-26.940
1000	2.239	0.887	2.676	0.747	-63.050
1420	1.754	1.402	2.979	0.585	-83.020
1441	1.732	1.425	2.984	0.578	-83.840
1460	1.711	1.445	2.988	0.571	-84.640
1500	1.669	1.489	2.995	0.557	-86.290
2000	1.218	1.931	2.914	0.406	-103.490
5000	0.279	2.771	1.670	0.093	-145.610
7500	0.129	2.895	1.163	0.043	-158.700
10000	0.074	2.940	0.886	0.025	-162.300
12000	0.052	2.959	0.742	0.017	-165.000

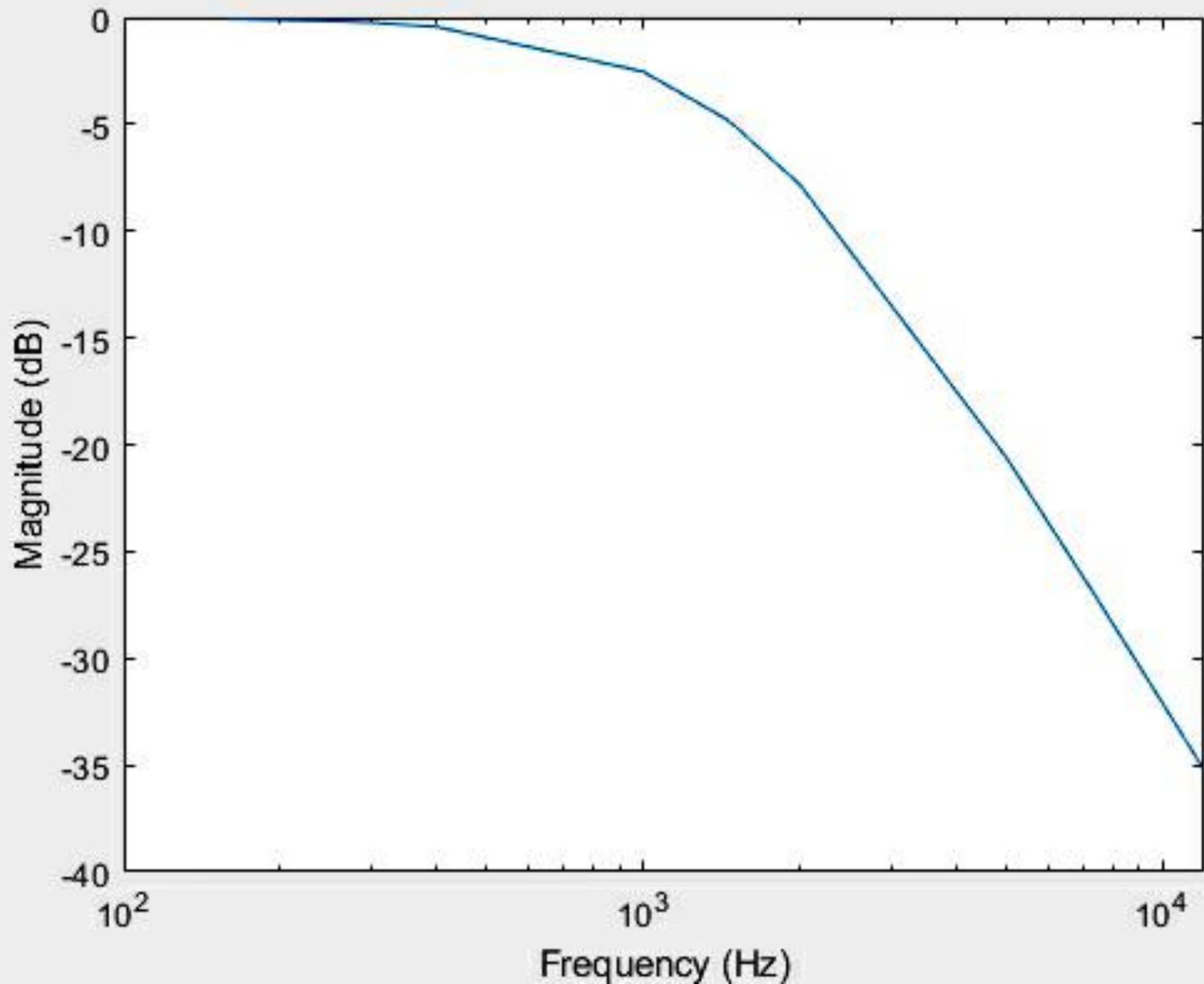

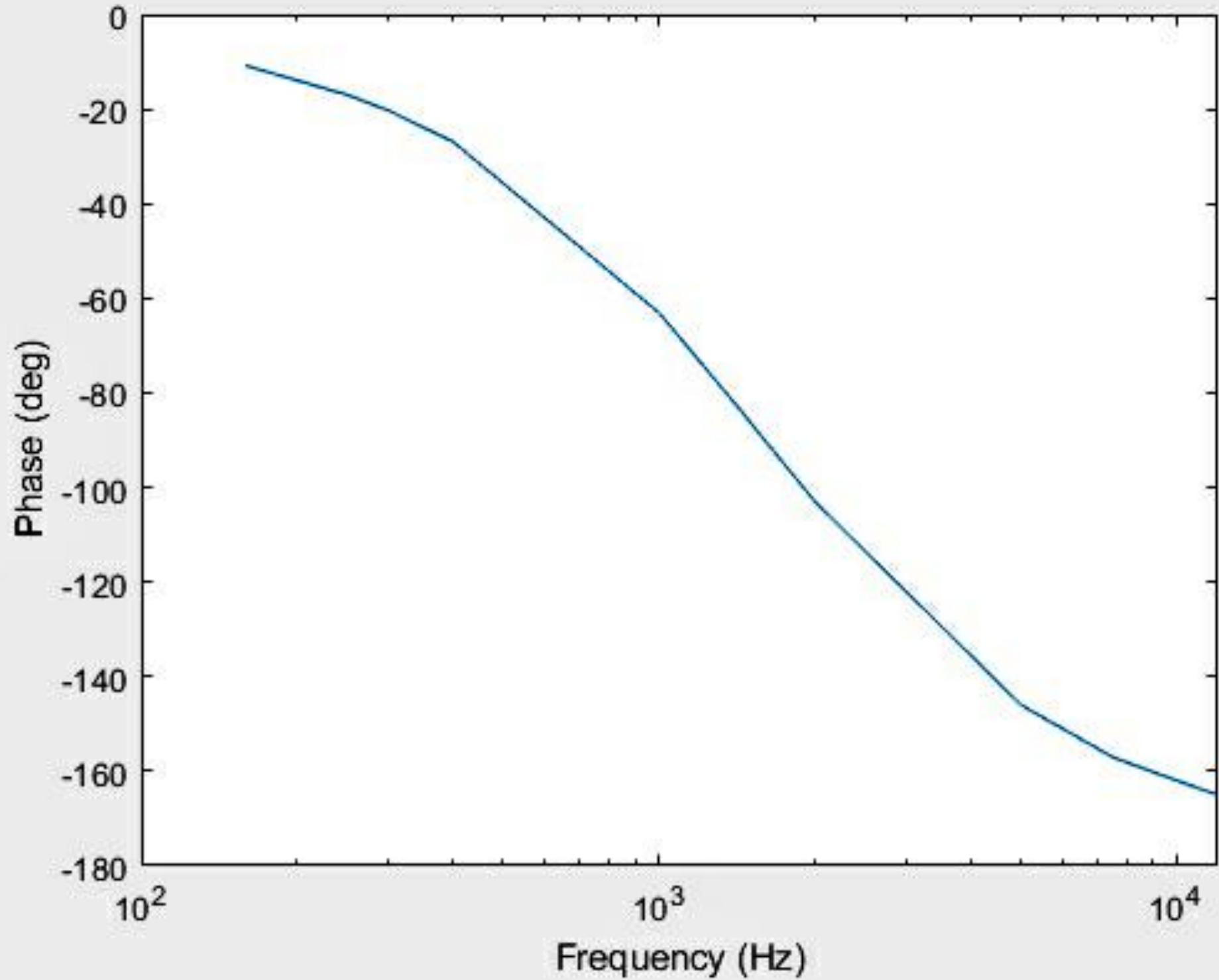

Bode Diagram

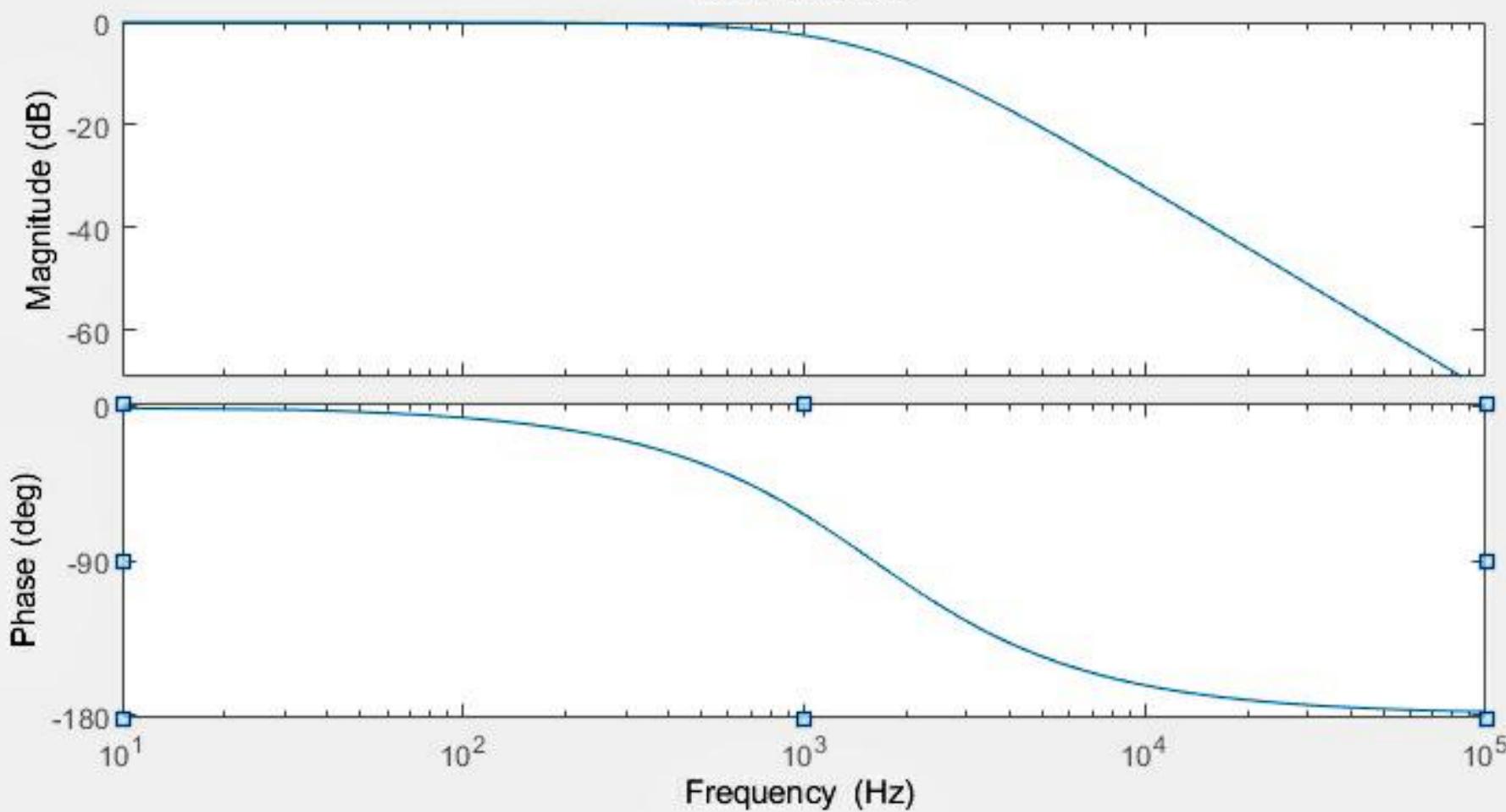

$$(i) \xi_p = 1.5 \Rightarrow R = 2000 \times 1.5 = 3000 \Omega$$

For input (V_{in}) = 3V (Amplitude) as sine waves

frequency (f) in Hz	V_c (in V)	N_L (in V)	N_R (in V)	Gain (V_c/V_{in})	Phase Degree
159	2.897	0.029	0.869	0.967	-16.780
250	2.767	0.069	1.306	0.924	-25.710
300	2.683	0.096	1.520	0.895	-30.300
400	2.488	0.158	1.883	0.832	-38.760
1000	1.513	0.599	2.857	0.505	-72.100
1420	1.115	0.892	2.992	0.372	-85.440
1441	1.100	0.905	2.993	0.367	-86.020
1460	1.086	0.918	2.995	0.363	-86.480
1500	1.058	0.944	2.998	0.353	-87.540
2000	0.785	1.244	2.965	0.262	-98.480
5000	0.231	2.291	2.181	0.077	-133.000
7500	0.117	2.616	1.660	0.039	-146.000
10000	0.069	2.786	1.315	0.023	-153.400
12000	0.049	2.831	1.122	0.017	-157.400

Calculations :


for (i), The maximum gain = 2.549 occurs at $f = 1500$ Hz
 $\therefore f_m = 1500$ Hz observed


$$\text{The maximum gain, theoretical} = \frac{1}{2 \xi_p \sqrt{1 - \xi_p^2}} = \frac{1}{2 \times 0.2 \sqrt{1 - 0.04}} = 2.552$$

$$f_m, \text{ theoretical} = \frac{\omega_n \times \sqrt{1 - 2\xi_p^2}}{2\pi} = 1527 \text{ Hz.}$$


(Since $\xi_p = 0.2$ and $\omega_n = 10^4$ rad/s)

$$\therefore \text{Percentage error in Maximum Gain} = \frac{|2.552 - 2.549|}{2.552} \times 100 \\ = 0.12\%$$

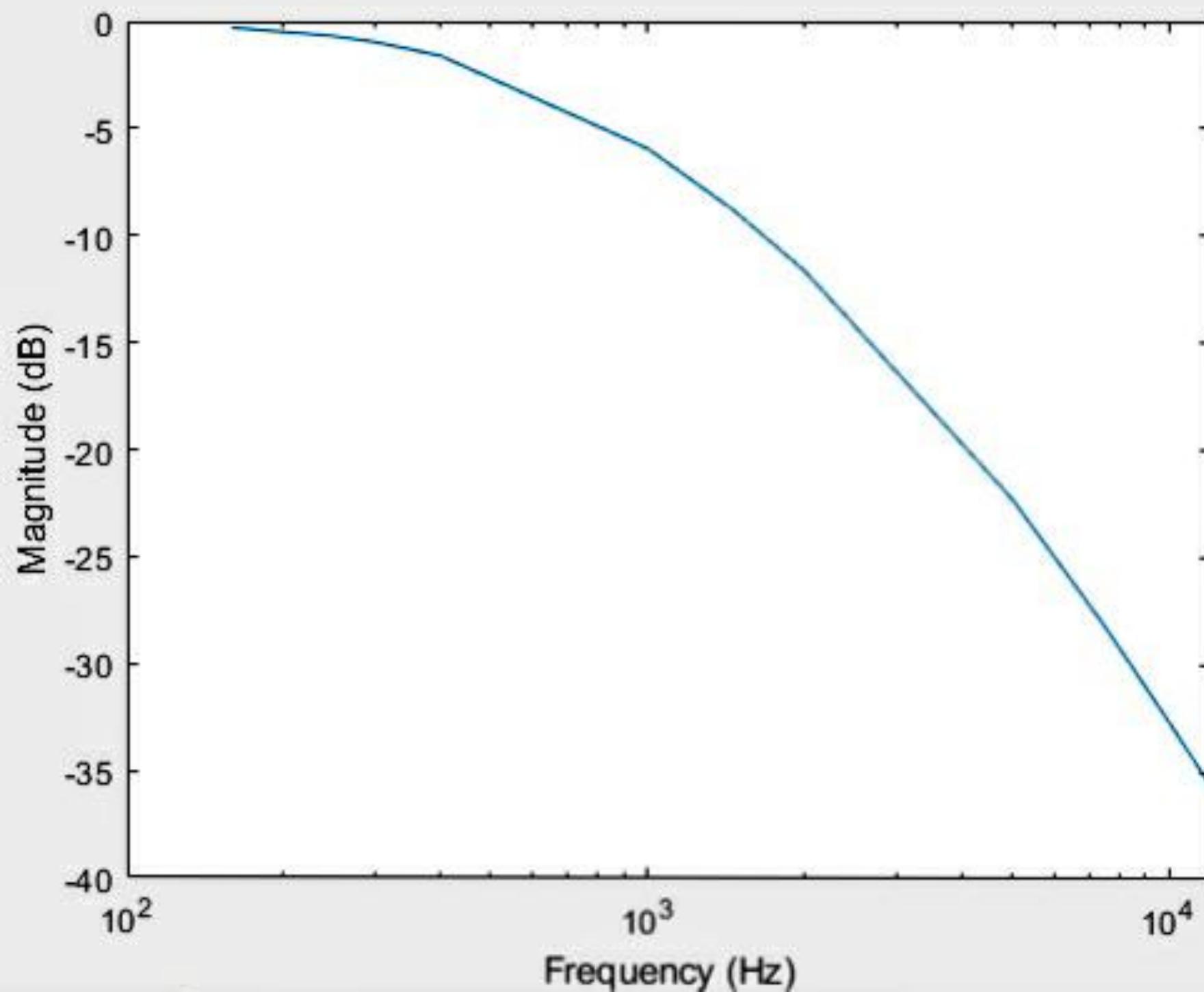

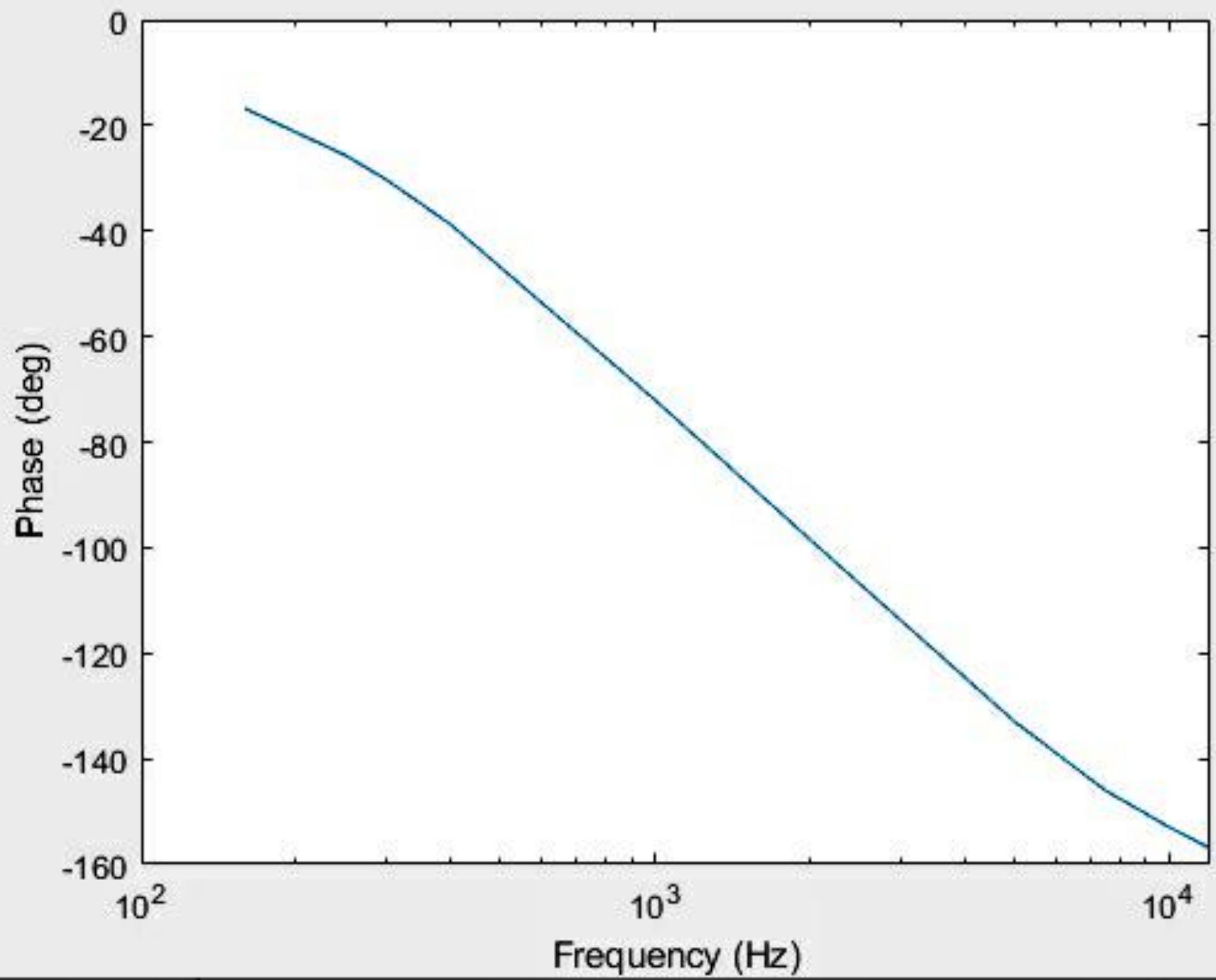

Bode Diagram

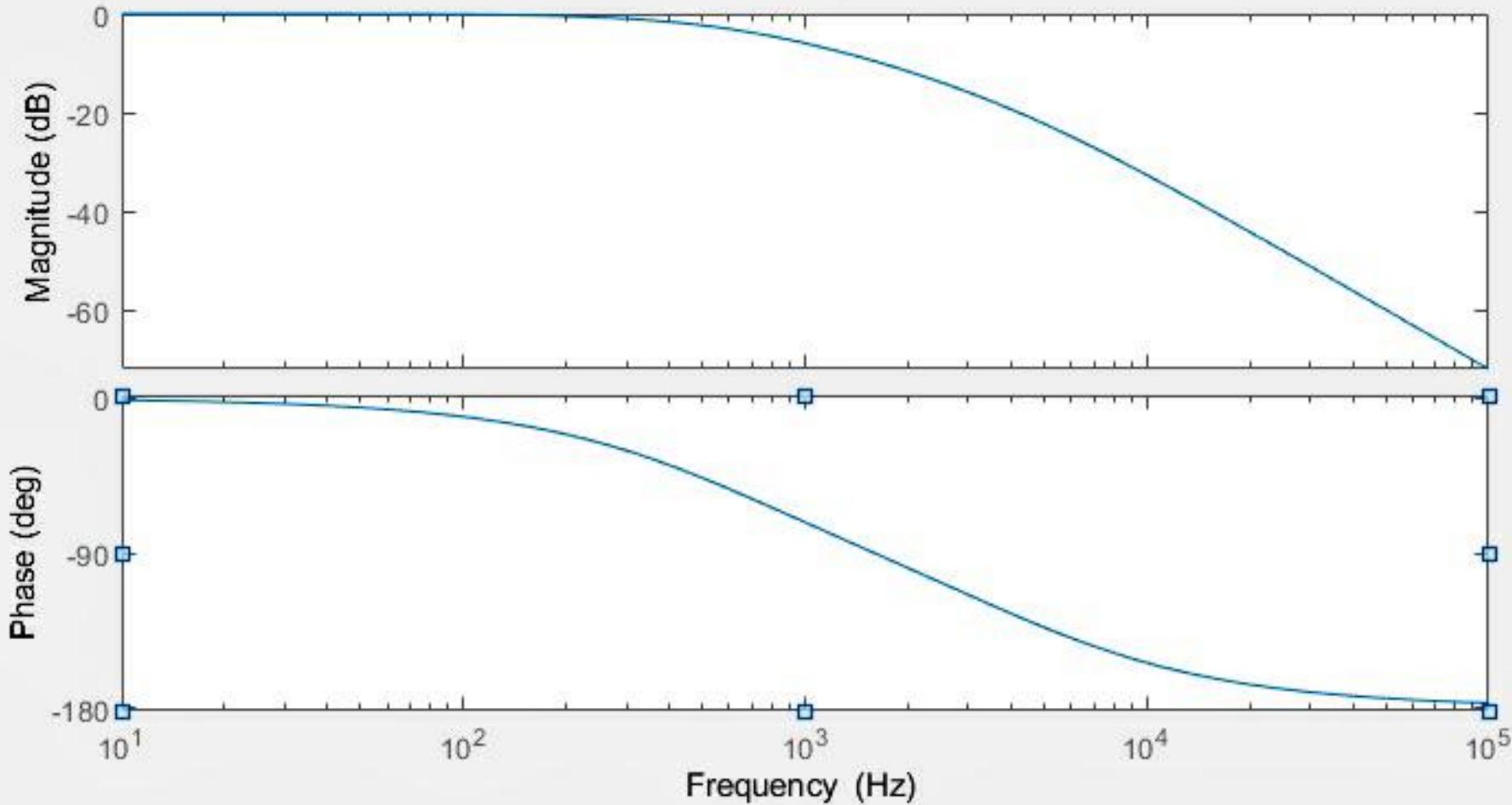

Percentage Error in ~~f_m~~ $f_m = \frac{|1527 - 1500|}{1527} \times 100\% = 1.77\%$

for (ii), The maximum gain, observed is 1.000 occurring at $f = 300\text{Hz}$.
 $\therefore f_m, \text{observed} = 250\text{ Hz}$

The maximum gain, theoretical $\frac{1}{2 \cdot \frac{\omega_n}{2\pi} \sqrt{1 - \left(\frac{\omega}{\omega_n}\right)^2}} = \frac{1}{2 \times 0.7 \sqrt{1 - 0.49}} = 1.000$

$$f_m, \text{theoretical} = \frac{\omega_n}{2\pi} \sqrt{1 - 2^2} = 225\text{ Hz}$$

\therefore Percentage error in maximum gain = $\frac{|1.000 - 1.000|}{1.000} \times 100\% = 0\%$

Percentage error in ~~f_m~~ $f_m = \frac{|250 - 225|}{225} \times 100 = 11.11\%$

for (iii) and (iv), there is no maximum gain, since they are monotonically decreasing gains.

Thus, they also do not have any f_m .

Discussions: This experiment enables us to define what are called filters. Since we do the experiment for an entire range of frequencies, we find that for the given circuit, some set of frequencies have a high gain they pass through the circuit, while some set of frequencies have a low gain (they do not pass through the circuit). This leads to the coining of several terms, like

- Low Pass Filter: only low frequencies pass through
- High Pass Filter: only high frequencies pass through

- Band Pass filter: Only the frequencies that lie within a certain band, pass through.
- Band Reject filter: All those frequencies that lie outside a certain band, pass through.

when we perform the experiment in real life, in the lab, we will expect a much higher error percentage, ~~because~~ because MATLAB ignores a lot of the non idealities of the real world, like extra resistances, capacitances and inductances, losses and many other factors. Also, the devices used to measure the voltages may give some error and thus overall error increases in a real life experiment and its accuracy decreases