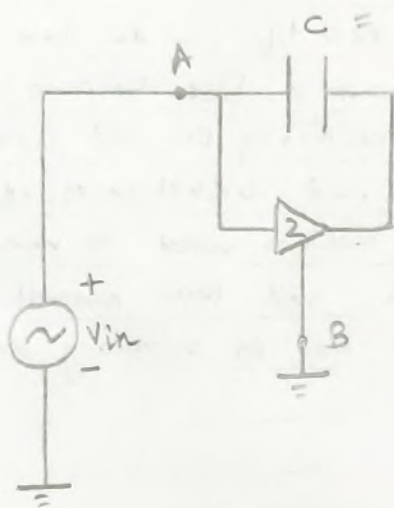


Experiment 5

Negative Impedance Converter (C to -C)



AB \rightarrow Terminals of negative Impedance Capacitor

Kaushal

for capacitance $(C) = 0.001 \mu F$,

Observation Table:

| frequency (f) (in Hz) | Applied Voltage Magnitude (in V) (Amplitude) | Current Magnitude (in A) (Amplitude) | Phase of current w.r.t voltage (in degree) | calculated Complex Impedence in $(-Z)$ |
|------------------------------|-------------------------------------------------------|-----------------------------------------------|--------------------------------------------------|-------------------------------------------------|
| 100 | 1 | 6.28×10^{-7} | 90° Lagging | $1592 \times 10^6 \angle 90^\circ$ |
| 200 | 1 | 1.25×10^{-6} | 90° Lagging | $8 \times 10^5 \angle 90^\circ$ |
| 300 | 1 | 1.88×10^{-6} | 90° Lagging | $5.319 \times 10^5 \angle 90^\circ$ |
| 500 | 1 | 3.13×10^{-6} | 90° Lagging | $3.195 \times 10^5 \angle 90^\circ$ |
| 1000 | 1 | 6.19×10^{-6} | 90° Lagging | $1.616 \times 10^5 \angle 90^\circ$ |
| 2000 | 1 | 12.32×10^{-6} | 90° Lagging | $8.117 \times 10^4 \angle 90^\circ$ |
| 4000 | 1 | 25.05×10^{-6} | 90° Lagging | $3.992 \times 10^4 \angle 90^\circ$ |
| 5000 | 1 | 31.29×10^{-6} | 90° Lagging | $3.196 \times 10^4 \angle 90^\circ$ |
| 7000 | 1 | 43.96×10^{-6} | 90° Lagging | $2.275 \times 10^4 \angle 90^\circ$ |
| 9000 | 1 | 56.53×10^{-6} | 90° Lagging | $1.769 \times 10^4 \angle 90^\circ$ |
| 10000 | 1 | 62.82×10^{-6} | 90° Lagging | $1.592 \times 10^4 \angle 90^\circ$ |

When we use this negative impedance circuit, to convert a capacitor to its negative ~~part~~, we get the formula of $X_C = \frac{-1}{j\omega C} = \frac{j}{\omega C}$.

Now for inductors, $X_L = jL\omega$.


When we equating X_L and X_C , we get $jL\omega = \frac{j}{\omega C} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$

Thus, even though, their phases are same, a negative cannot mimic an inductor for all the values of the frequencies. It can act as an inductor for only $\omega = \frac{1}{\sqrt{LC}}$. Thus, we cannot create an inductor using

a capacitor (or vice-versa) using this negative impedance converter. For that, we need to use a gyrator.

Kanshal

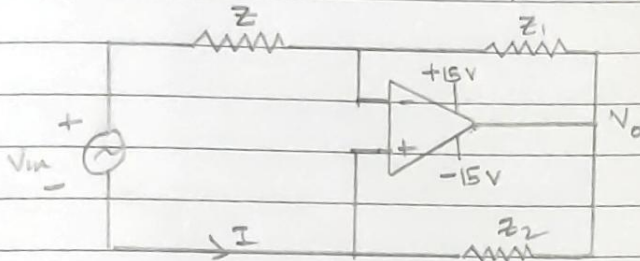But, if we use the ~~new~~ circuit, as shown in the manual, i.e.,



$$\text{Then } V_o = V_{in} \left(1 + \frac{Z_1}{Z_2} \right) \Rightarrow V_{in} - V_o = -V_{in} \left(\frac{Z_1}{Z_2} \right) \quad \text{--- (1)}$$

Also, $\Rightarrow V_{in} - V_o = I Z_2$ (Since Op Amps takes 0 input current)
 Now $Z_{\text{input}} = \frac{V_{in}}{I} = \text{--- (2)}$ (So voltage drop across Z_1 is 0)
 --- (3)

Dividing (1) and (2)
 $\Rightarrow 1 = - \frac{V_{in} \left(\frac{Z_1}{Z_2} \right)}{I Z_2}$

$$\Rightarrow Z = \frac{V_{in}}{I} = -Z \left(\frac{Z_1}{Z_2} \right)$$

From (3) $\Rightarrow Z_{\text{input}} = -Z \left(\frac{Z_2}{Z_1} \right)$

Now we usually take $Z_1 = Z_2$ to get negative impedance ($-Z$)
 But now we can make Z and Z_2 as resistors and Z_1 as our capacitor.
 $\Rightarrow Z_{\text{input}} = -R \cdot \frac{R}{\left(\frac{1}{j\omega C} \right)} = -R^2 j\omega C = + \frac{R^2 \omega C}{j}$

Now, we feed this Z_{input} to a normal negative impedance converter and get $Z_{\text{final}} = -Z_{\text{input}} = - \frac{R^2 \omega C}{j} = j(R^2 \omega C)$

If we take $R^2 C = L$, then we get, $Z_{\text{final}} = j(\omega L)$
 which is the expression for an inductor.

So its possible to convert a capacitor to an inductor.

$|Z|$ vs f for Negative Impedance Converter (C to -C)

Scale:


On X-axis:

1cm = 1000 Hz

On Y-axis:

1cm = $10^5 \Omega$


Magnitude of Impedance ($|Z|$) in $\Omega \times 10^4 \rightarrow$

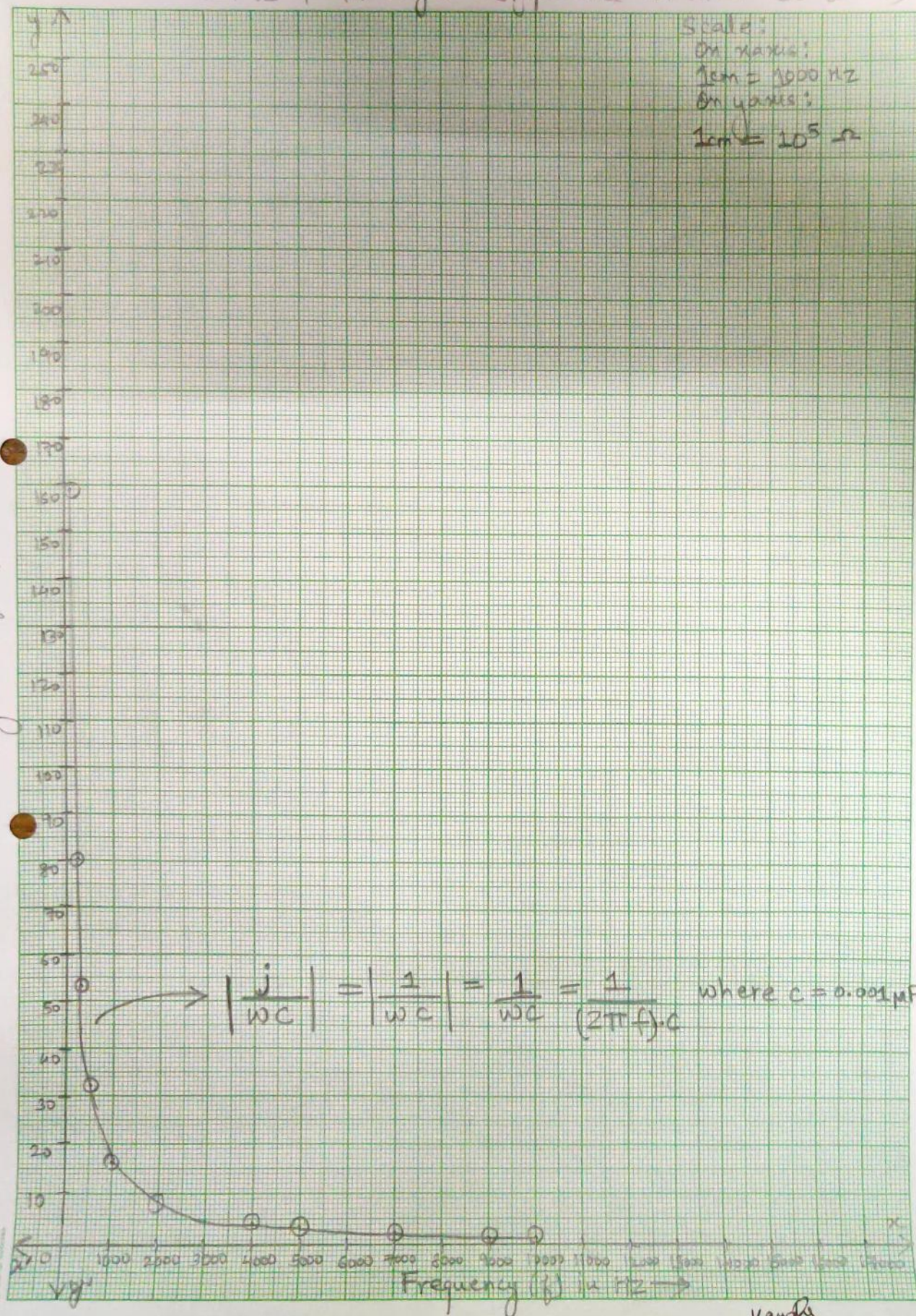


Kanishk


Scale:
 On x-axis:
 $1\text{cm} = 1000\text{ Hz}$
 On y-axis:
 $1\text{cm} = 10\text{ Degrees}$

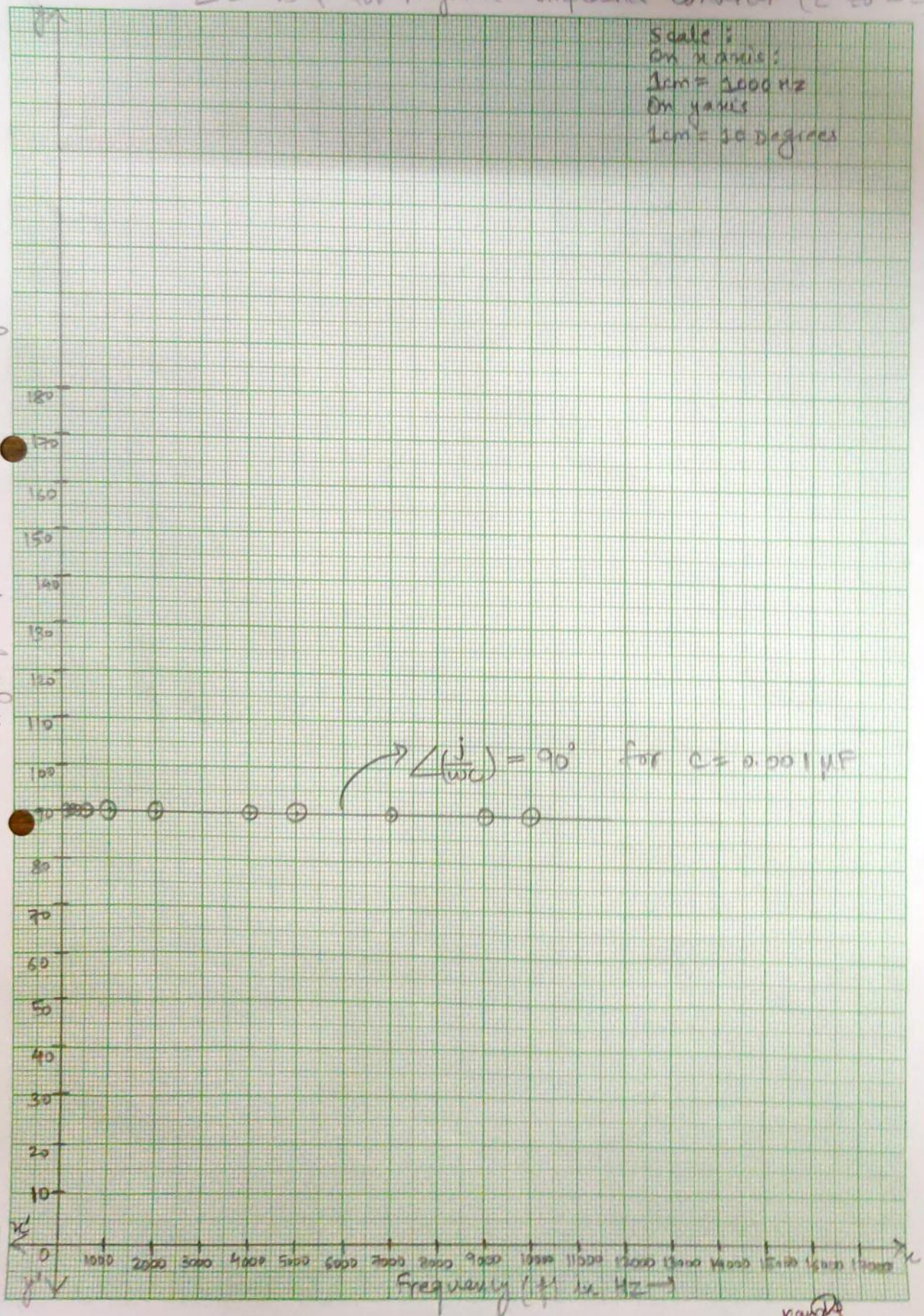Angle of Impedance ($\angle Z$) in degrees \rightarrow



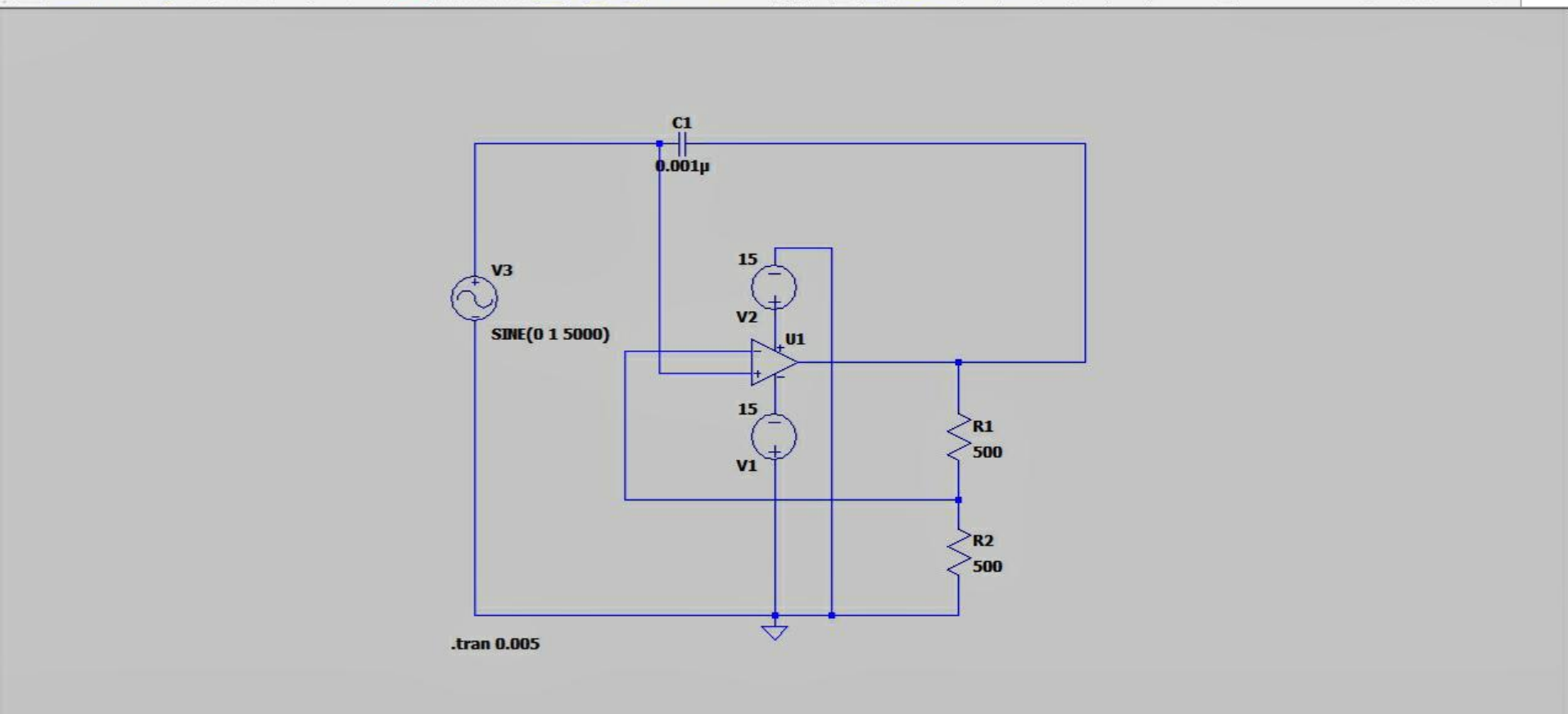

Gyrator, (Capacitance to Inductance)

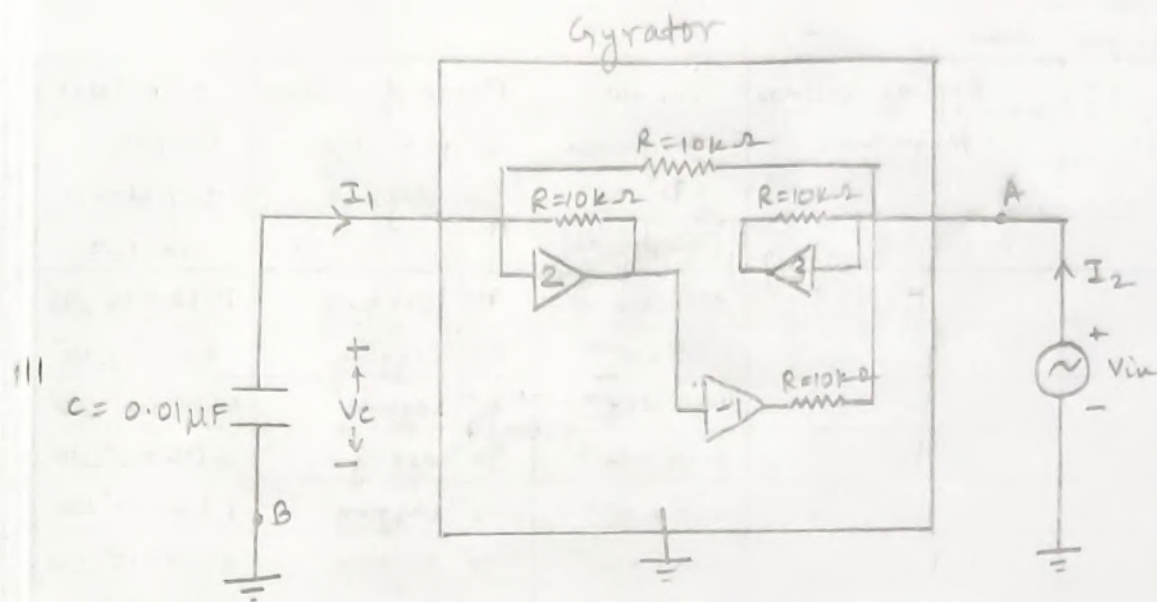

AB \rightarrow Terminals of the constructed Inductor.

Kaushal

From the two-port network representation of the gyrator, we have the following equations,

$$V_C = -RI_2 \quad \text{and} \quad V_{in} = RI_1 \quad (\text{where } R \text{ is value of the resistances used in the gyrator})$$

(NOTE: R is not the value of the resistances used in the op-amps)

Now, in Laplace Domain, we replace c by $1/(cs)$ and consider it as an impedance.

$$\therefore V_c = (-I_1) \left(\frac{1}{cs} \right) \quad \text{--- (3)}$$

Now, we calculate the Impedance for the "Inductor + Capacitor" part.

$$\Rightarrow Z = \frac{V_{in}}{I_1}$$

$$Z = \frac{R I_1}{I_1} \quad (\text{from } \textcircled{2})$$

$$Z = \frac{R I_1}{\left(\frac{-V_c}{R} \right)} \quad (\text{from (1)})$$

$$\underline{Z = -R^2 \underline{I_1}}_{V_C}$$

$$Z = - \frac{\mu^2 I_1}{(I_1) \left(\frac{1}{cs} \right)} \quad (\text{from (3)})$$

$$Z = R^2 C S$$

If we substitute R^2C by L , then we have

$$Z = Ls \quad (\text{where } L = R^2 C) \quad (\text{This is the Laplace domain impedance of } R^2 C)$$

Thus, we get an effective inductor, with inductance $(L) = R^2 C$, by connecting a capacitor to a gyrator.

Kaushik

For capacitance $(C) = 0.01 \mu F$ and $R = 10 k\Omega$ ($\therefore L = 1 H$)

Observation Table:

($\therefore L = R^2 C$)


| Frequency (f) (in Hz) | Applied Voltage Magnitude (in V) (Amplitude) | Current Magnitude (in A) (Amplitude) | Phase of current w.r.t. voltage (in degree) | Calculated Complex Impedance (in Ω) |
|--------------------------|-------------------------------------------------------|-----------------------------------------------|---------------------------------------------------|------------------------------------------------------|
| 300 | 1 | 522.86×10^{-6} | 90° Lagging | $1912.56 \angle 90^\circ$ |
| 500 | 1 | 312.93×10^{-6} | 90° Lagging | $3195.60 \angle 90^\circ$ |
| 1000 | 1 | 158.76×10^{-6} | 90° Lagging | $6298.82 \angle 90^\circ$ |
| 2000 | 1 | 79.40×10^{-6} | 90° Lagging | $12594.46 \angle 90^\circ$ |
| 4000 | 1 | 39.57×10^{-6} | 90° Lagging | $25271.67 \angle 90^\circ$ |
| 5000 | 1 | 31.57×10^{-6} | 90° Lagging | $31675.64 \angle 90^\circ$ |
| 7000 | 1 | 22.39×10^{-6} | 90° Lagging | $44662.80 \angle 90^\circ$ |
| 9000 | 1 | 17.22×10^{-6} | 90° Lagging | $58072.01 \angle 90^\circ$ |
| 10000 | 1 | 15.43×10^{-6} | 90° Lagging | $64808.81 \angle 90^\circ$ |

NOTE: Here, the amplitude = $(I_{max} - I_{min})$. Also, the frequency is taken from 300 Hz, instead of 100 Hz, ² since from 100 Hz to around 250 Hz, the output current is not sinusoidal.

Kavshal

Magnitude of Impedance ($|Z|$) in $\Omega \times 10^3$

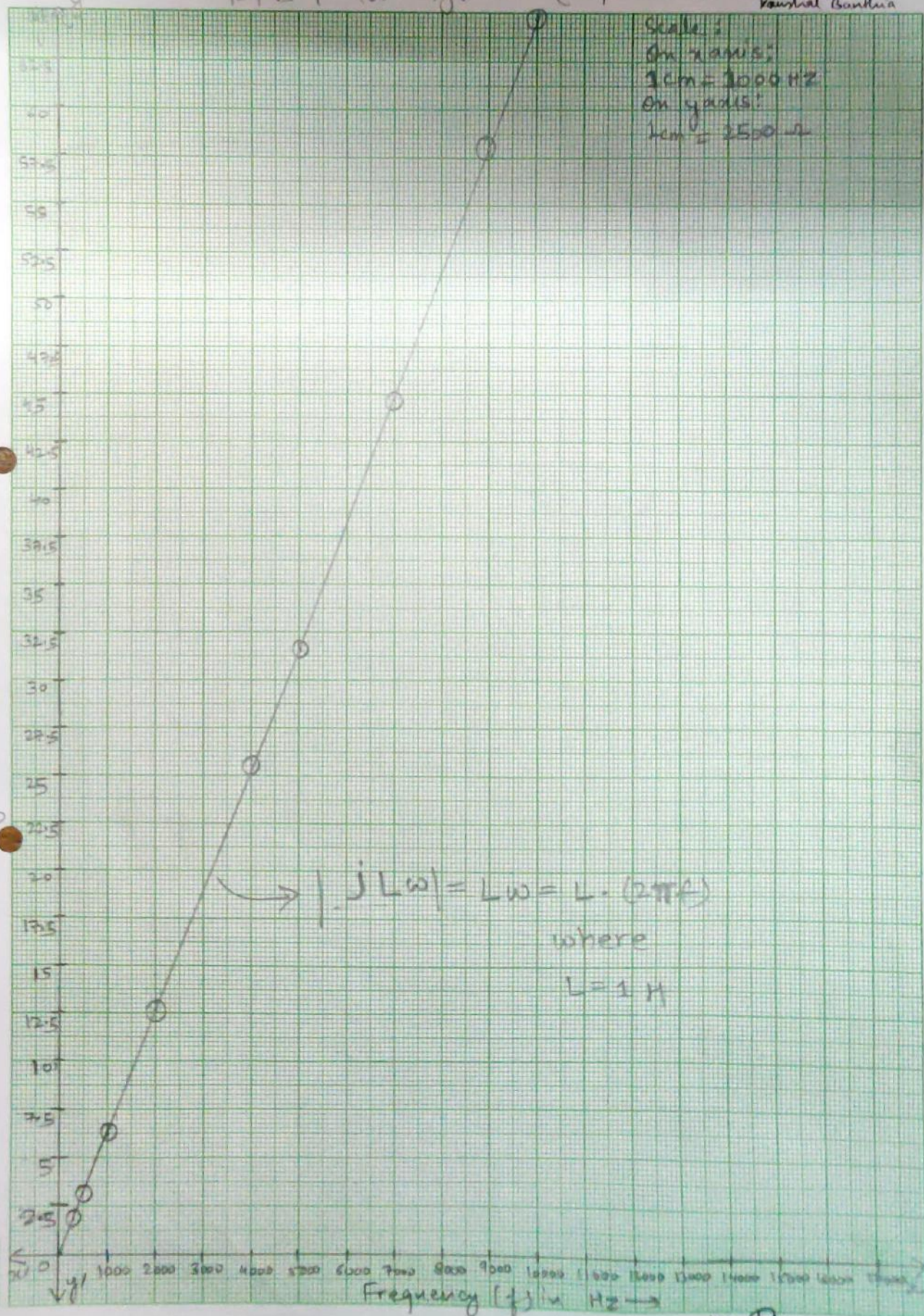
Scale:
On x axis:
1cm = 1000 Hz
On y axis:
1cm = 2500 Ω



Raunhal

Angle of Impedance ($\angle Z$) in degrees \rightarrow

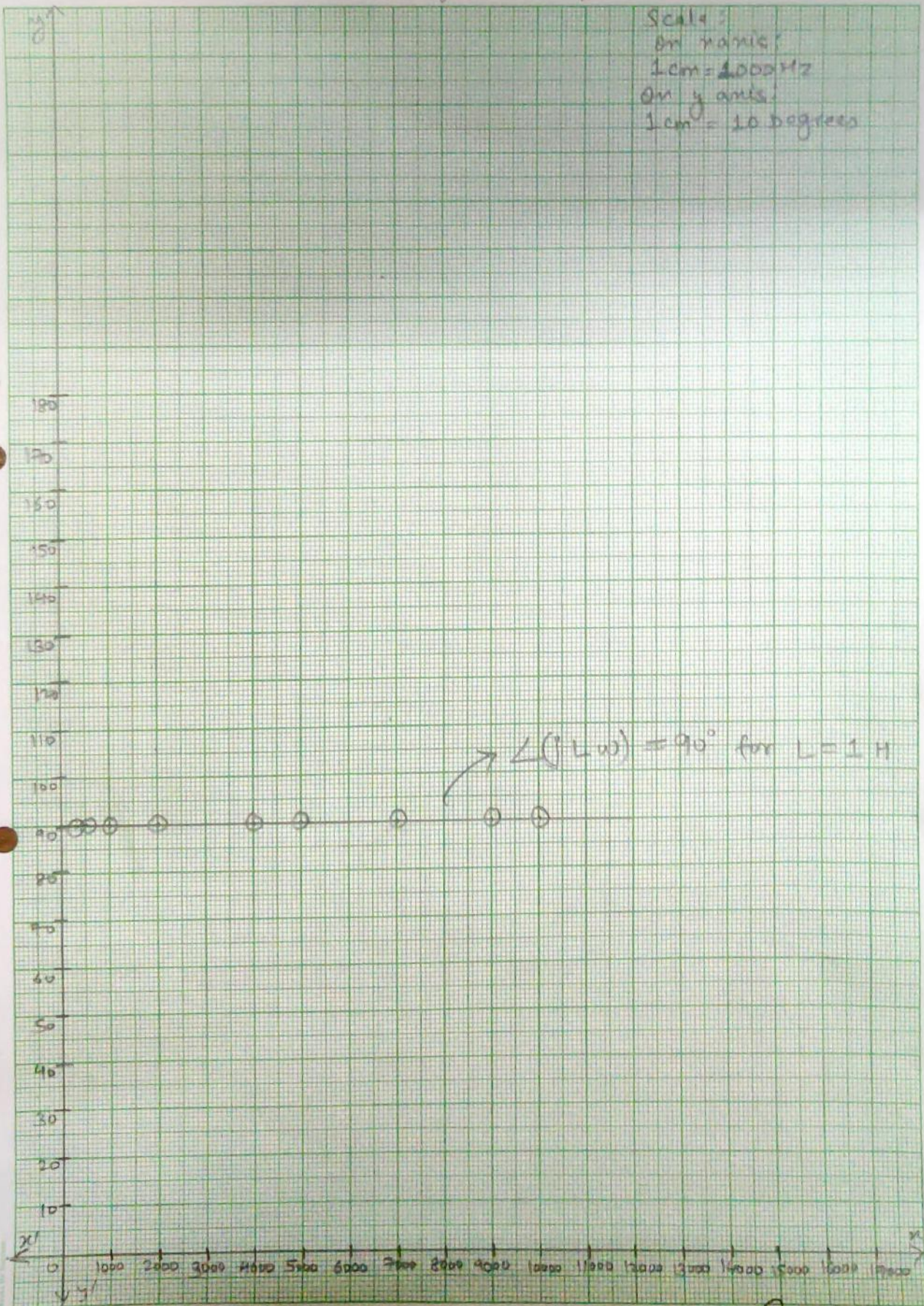Scale:
On x-axis:
1cm = 1000 Hz
On y-axis:
1cm = 10 degrees



range

